

PHY2250 - Electronics & Circuit Theory, Spring '09 Practice Exam

Name: Dr. Hawley

Turn off (OFF) all cell phones
Answer on these papers

Part I (72 points): Circle the "best" answer. No need to show your work.

1. (4 points) The smallest unit of an element is: (circle one)

- a) An electron
- b) A molecule
- c) A compound
- d) An atom

2. (4 points) In a series RC circuit:


- a) The current flowing in the circuit lags the voltage across the capacitor by 90 degrees.
- b) The circuit current and resistor voltage are in phase with one another
- c) The current leads the voltage by 45 degrees
- d) All of the above
- e) Both (a) and (b), but not (c)

3. (4 points) What are the majority carriers in an N-type semiconductor?

- a) Positrons
- b) Electrons
- c) Holes
- d) Protons


4. (4 points) The following diagram of a diode and variable resistor can serve as a model of what electronic component? (circle one)

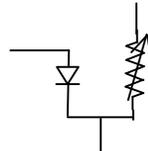- a) capacitor
- b) op-amp
- c) transistor
- d) regulator



5. (4 points) The op-amp circuit shown the right is a/an (circle one)

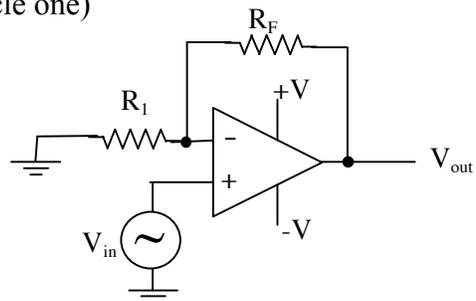- a) Closed-loop noninverting amplifier
- b) Active high-pass filter
- c) Open-loop signal generator
- d) Closed-loop inverting amplifier



Los Angeles, CA. In a drug deal gone horribly wrong, rising hip-hop star "KillahWatt" lodged his "grill" across the output terminals of a step-down transformer putting out 20A at 240V RMS.


6. (4 points) Calculate the average power coursing through his grill.

- a) 12 W
- b) 120 W
- c) 2880 W
- d) 4800 W

7. (4 points) Calculate the impedance of said grill.

- a) 2 Ω
- b) 8 Ω
- c) 12 Ω
- d) 4800 Ω

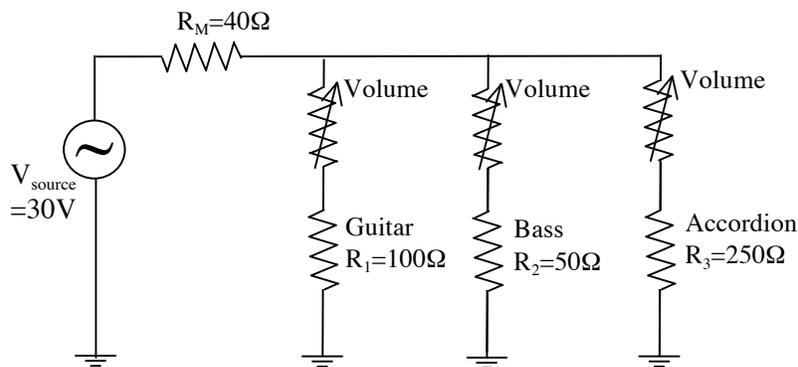23. (10 points) In the following "pseudo-cue-system," three instrument channels are placed in parallel, and each channel has a volume knob (represented by variable resistors).



a) Say the guitar channel's volume knob is "all the way on", i.e. zero resistance, and the other two volume knobs are turned "off," i.e. "infinite" resistance. What is...

...the total current?

...the current that flows through the guitar channel?

...the voltage across the guitar?

$$I_T = V_S / (R_M + R_1) = 30 / 140 = 0.214 \text{ A}$$

I_1 is the same as I_T

$$V_1 = I_1 * R_1 = 0.214 * 100 = 21.4 \text{ V}$$

b) Now suppose the bass channel's knob is also turned all the way on....

What is the total current?

What is the current through the guitar channel?

What is the voltage across the guitar?

$$R_{12} = (1/R_1 + 1/R_2)^{-1} = 100/3 = 33.3 \text{ Ohms}$$

$$R_T = R_M + R_{12} = 40 + 33.3 = 73.3 \text{ Ohms}$$

$$I_T = 30 \text{ V} / 73.3 \text{ Ohms} = 0.409 \text{ A} \quad \text{Note: greater than in part (a), because added a current-path}$$

$$I_1 = I_T * (R_{12} / R_1) = .409 * (33.3 / 100) = 0.136 \text{ A}$$

$$V_1 = I_1 * R_1 = 13.6 \text{ V}$$

Extra Credit:

10. (2 points) Which recording industry pioneer "accidentally" created the first diode, but could not see any practical application of it?

Thomas Edison

11. (2 points) How badly would you like to be a laboratory assistant for PHY2250 in Fall '09?