

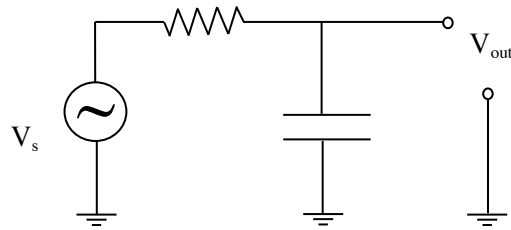


**PHY2250 "Homework 6". Dr. Hawley's answers.**

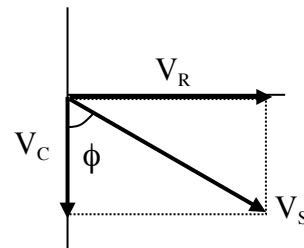
1. Part of the crossover for a 2-way loudspeaker system has a capacitance of  $2 \mu\text{F}$  and a resistance of  $1 \text{ k}\Omega$ , and has the following schematic:



- What is the time constant  $\tau$  for this part of the circuit?
  - Calculate the turnover frequency  $f_0 = 1/(2\pi\tau)$  and explain briefly what happens to the ratio  $V_{\text{out}}/V_s$  (just the amplitudes, ignore phase effects) for freq's above & below this frequency.
  - Which signals are phase-shifted more relative to the source voltage: low or high frequencies?
  - Calculate the phase shift in degrees from  $V_s$  to  $V_{\text{out}}$  for a 150 Hz sine wave. Include the sign (+ or -) of the shift to indicate leading or lagging.
- Hint: Use a phasor diagram!

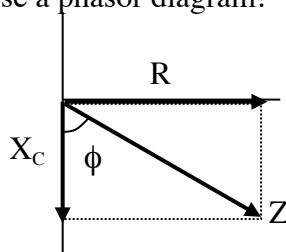


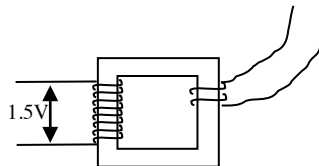2. A signal from a mic is coming in at 20mV. It then connects to a transformer... What turns ratio is needed to step the voltage up to 1.5V (assuming an ideal transformer)?



- Describe Faraday's Law of induction, and list three different examples of how it arises (or is used) in audio engineering.
- Given your answer to #3, would you expect induction to be a more significant effect at *high* or *low* frequencies, and why?
- Some people like to say that "an inductor is like the opposite of a capacitor." Describe in what sense(s) this can be true.


6.

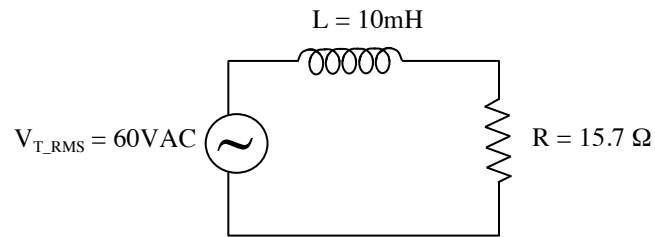

For the circuit shown, find

- a)  $V_T$  (peak)
- b) For the frequency  $f = 63$  Hz, find
  - i.  $X_L$
  - ii.  $Z_T$
  - iii. The angle  $\theta$  between  $Z_T$  and  $R$ .
  - iv.  $V_R$
- c) Repeat (b) for  $f = 250$  Hz
- d) Repeat (b) for  $f = 2000$  Hz

7. Notch Filter

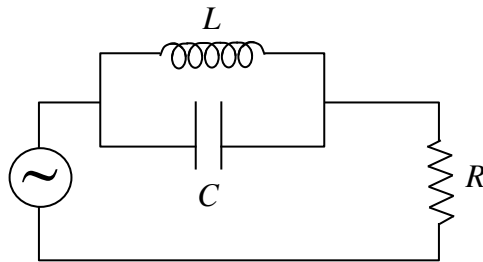

In the schematic shown,  $V_T = 100$  V,  $L = 100$  mH,  $C = 10$   $\mu$ F, and  $R = 8$   $\Omega$ .

- a) At what frequency  $f_n$  is  $X_C = X_L$ ?
- b) Show that the impedance value at this frequency is equal to  $X_n = \sqrt{L/C}$  and find the value of  $X_n$

8. Do the exercise at the end in the Phasor Diagram handout. (Answers at bottom of handout.)