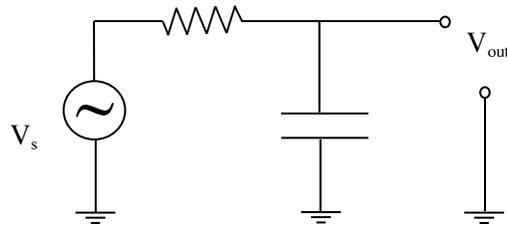



PHY2250 "Homework 6". Dr. Hawley's answers.

1. Part of the crossover for a 2-way loudspeaker system has a capacitance of $2 \mu\text{F}$ and a resistance of $1 \text{ k}\Omega$, and has the following schematic:



- What is the time constant τ for this part of the circuit?
- Calculate the turnover frequency $f_0 = 1/(2\pi\tau)$ and explain briefly what happens to the ratio V_{out}/V_s (just the amplitudes, ignore phase effects) for freq's above & below this frequency.
- Which signals are phase-shifted more relative to the source voltage: low or high frequencies?
- Calculate the phase shift in degrees from V_s to V_{out} for a 150 Hz sine wave. Include the sign (+ or -) of the shift to indicate leading or lagging.

Hint: Use a phasor diagram!

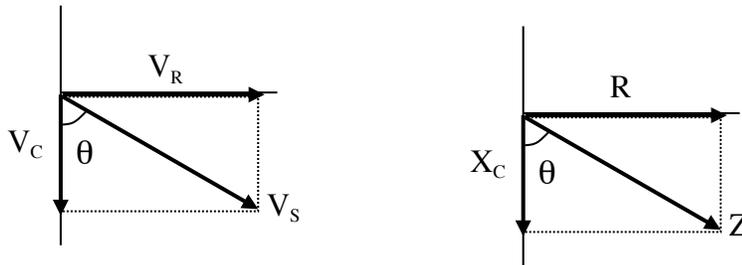

Answer:

a. $\tau = RC = (1000)(2 \cdot 10^{-6}) = 2\text{ms}$

b. $f_0 = 1/(2\pi\tau) = 79.6\text{s}$. Below this, the amplitude doesn't depend much on frequency. Above f_0 , the frequency falls off like $1/f$.


c. High frequencies.

d. $X_c = 1/(2\pi fC) = 1/((2\pi)(150)(2 \cdot 10^{-6})) = 531\Omega$

$$\theta = \tan^{-1}(R/X_c) = \tan^{-1}(1000/531) = -62.0^\circ$$

where we've tacked on the - sign to indicate lagging.

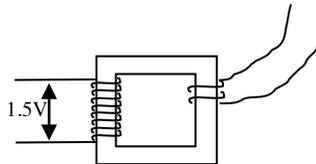2. A signal from a mic is coming in at 20mV. It then connects to a transformer... What turns ratio is needed to step the voltage up to 1.5V (assuming an ideal transformer)?



Answer:

$$V_2 = nV_1, \text{ where } n = \frac{N_2}{N_1}.$$

$$n = \frac{V_2}{V_1} = \frac{1.5V}{0.02V} = 75$$

3. Describe Faraday's Law of induction, and list three different examples of how it arises (or is used) in audio engineering.

Answer: A time-changing magnetic flux induces a voltage in a loop of wire. The direction of the induced current is so as to oppose the change in flux. Examples: dynamic microphones, play heads, transformers, guitar pickups.

4. Given your answer to #3, would you expect induction to be a more significant effect at *high* or *low* frequencies, and why?

Answer: High frequencies, because with higher frequencies the flux is changing faster than for low frequencies.


5. Some people like to say that "an inductor is like the opposite of a capacitor." Describe in what sense(s) this can be true.

Answer:

Phase: Inductor voltage is 90° ahead of the current, whereas capacitor voltage is 90° behind the current.

Frequency dependence: Inductive reactance is proportional to frequency, whereas capacitive reactance is inversely proportional to frequency.

6.

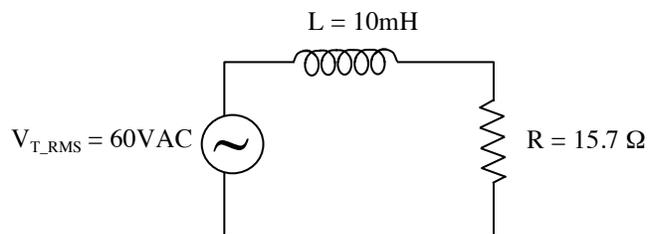

For the circuit shown, find

a) V_T (peak)

$$V_T = V_{T,RMS} / 0.707 = 84.9 \text{ V}$$

b) For the frequency $f = 63 \text{ Hz}$, find

i. $X_L = 2\pi fL = 2\pi(63 \text{ Hz})(0.01 \text{ H}) = 3.96 \Omega$

ii. The angle θ between Z_T and R , and the cosine of θ .

$$\theta = \tan^{-1}(X_L / R) = \tan^{-1}(3.96 / 15.7) = 14.16^\circ$$


$$\cos\theta = 0.9696$$

iii. $Z_T = \sqrt{R^2 + X_L^2} = 16.2 \Omega$

iv. $V_R = V_T \cos\theta = 82.3 \text{ V}$

- c) Repeat (b) for $f = 250$ Hz
- $X_L = 15.7 \Omega$
 - $\theta = 45.0^\circ$, $\cos\theta = 0.7069$
 - $Z = 22.2 \Omega$
 - $V_R = 60V$
- d) Repeat (b) for $f = 2000$ Hz
- $X_L = 125.6 \Omega$
 - $\theta = 82.9^\circ$, $\cos\theta = 0.1240$
 - $Z = 126.6 \Omega$
 - $V_R = 10.5 V$

7. Notch Filter

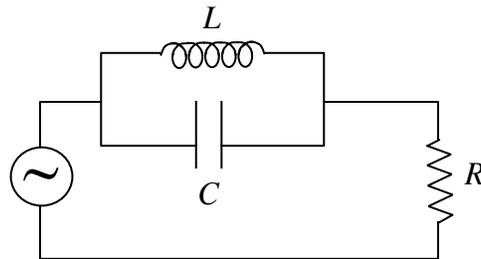

In the schematic shown, $V_T = 100$ V, $L = 1$ mH, $C = 0.1$ mF, and $R = 8 \Omega$.

- a) At what frequency f_n is $X_C = X_L$?
- $$f_n = \frac{1}{2\pi\sqrt{LC}} = 503 \text{ Hz}$$
- b) Show that the impedance value at this frequency is equal to $X_n = \sqrt{L/C}$ and find the value of X_n
- $$X_n = 10 \Omega$$

8. Do the exercise at the end in the Phasor Diagram handout. (Answers at bottom of handout.)