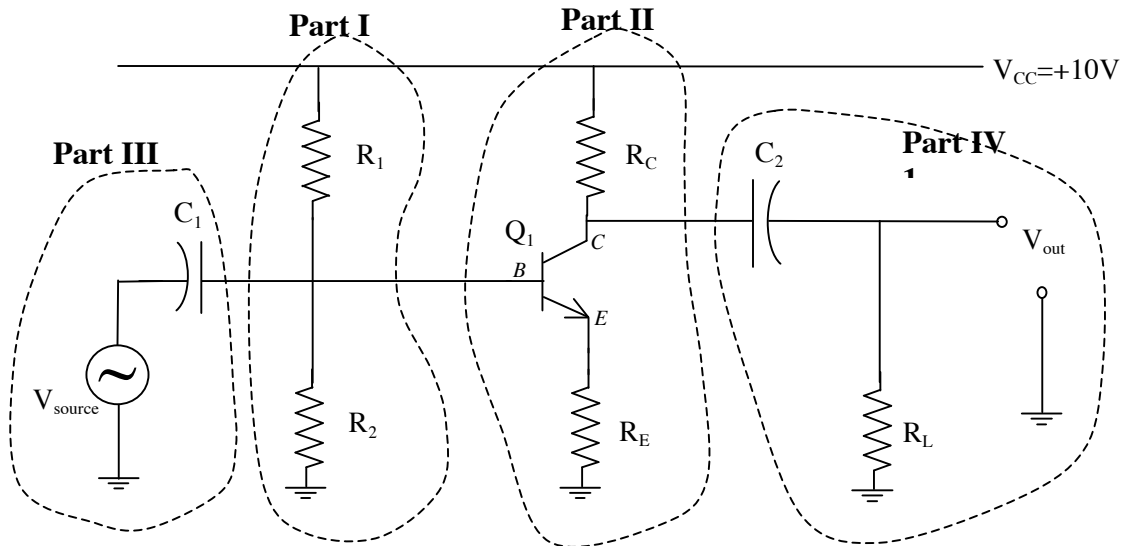


**PHY2250 - HW 8 Answers**

- (1 point) In a given transistor circuit, the emitter current is 25mA and the collector current is 24.6mA. What is the base current? **Answer: 0.4 mA**
- (4 points) In the following amplifier schematic,  $R_1=5k\Omega$ ,  $R_2=2k\Omega$ ,  $R_C=1k\Omega$  and  $R_E=500\Omega$ .



- Referring to "Part I", what is  $V_B$ , the DC voltage at the transistor's base?  
**Answer:  $V_B = V_{CC} * R_2 / (R_1 + R_2) = 10 * 2/7 = 2.86 V$**
- What is  $V_E$ , the voltage at the emitter?  
**Answer:  $V_E = V_B - 0.7V = 2.16 V$**
- Given  $V_E$ , what are  $I_E$  and  $I_C$ ? (Use  $\beta_{DC}=100$ .)  
**Answer:  $I_E = V_E / R_E = 2.16 / 500 = 4.32 mA$**   
 **$I_C = I_E * \beta_{DC} / (\beta_{DC} + 1) = 3.42 * 100/101 = 4.28 mA$**
- What are the role of the capacitors  $C_1$  and  $C_2$ ? i.e. why might you want them there?  
**Answer: They "block" any DC bias from flowing between Parts I and III, and Parts II and IV, respectively.**

- In the text, Chapter 28, Question 5. Derive the equation  $\alpha_{DC} = \beta_{DC} / (\beta_{DC} + 1)$

$$I_E = I_B + I_C = \left( \frac{I_C}{\beta_{DC}} \right) + I_C = I_C \left( \frac{1}{\beta_{DC}} + 1 \right) = I_C \left( \frac{1}{\beta_{DC}} + \frac{\beta_{DC}}{\beta_{DC}} \right)$$


$$I_E = I_C \left( \frac{1 + \beta_{DC}}{\beta_{DC}} \right)$$

$$I_E \left( \frac{\beta_{DC}}{1 + \beta_{DC}} \right) = I_C$$

$$\therefore \alpha_{DC} \equiv \frac{I_C}{I_E} = \frac{\beta_{DC}}{1 + \beta_{DC}}$$

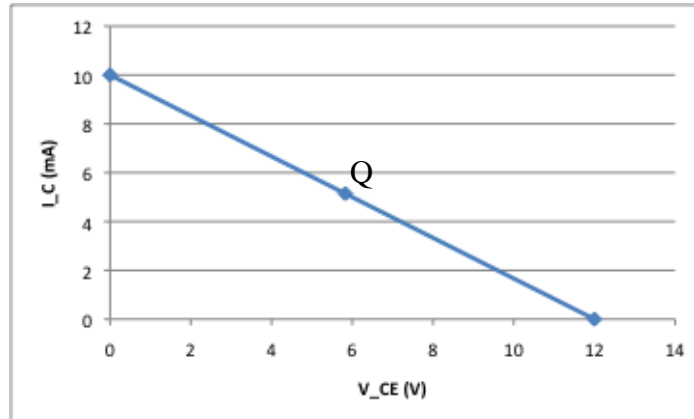4. Problem 28-30

**Answer:**  $I_{C(sat)} = V_{CC} / R_C = 12/1200 = 10 \text{ mA}$   
 $V_{CE(off)} = V_{CC} = 12 \text{ V}$   
 $I_{BQ} = (V_{CC} - 0.7V) / R_B = 11.3 / 220000 = 51.4 \mu\text{A}$   
 $I_{CQ} = I_{BQ} * \beta_{DC} = 5.14 \text{ mA}$   
 $V_{CEQ} = V_{CC} - I_{CQ}R_C = 5.83 \text{ V}$



5. Problem 28-38

**Answer:**  
a.  $V_B = V_{CC} R_2 / (R_1 + R_2) = 10 * 3.3 / (3.3+8.2) = 2.87 \text{ V}$   
b.  $V_E = V_B - 0.7V = 2.17 \text{ V}$   
c.  $I_E = V_E / R_E = 2.17 / 750 = 2.89 \text{ mA}$   
 $I_{CQ} = I_E \beta / (\beta+1) = 2.87 \text{ mA}$   
d.  $V_{CQ} = V_{CC} - I_C R_C = 10 - 2.87V = 7.13V$   
e.  $V_{CEQ} = V_C - V_E = 4.96 \text{ V}$   
f.  $I_{C(sat)} = V_{CC} / (R_C + R_E) = 10 / 1750 = 5.71 \text{ mA}$   
e.  $V_{CE(off)} = 10V$

6. What is the function of capacitor  $C_E$  in the circuit shown in Figure 29-3?

**Answer:** This provides the AC part of the signal with "a low impedance path to ground," meaning it allows AC signals to *bypass*  $R_E$  -- thereby increasing the AC gain of the amplifier -- without changing the DC part or "Q point."