

**PHY2250- HW 9 – Op Amps - Answers.**


1. (1 point) What is "slew-rate distortion" and when does it occur? (Some of you saw this in lab.) Feel free to refer to your text.

**Slew rate distortion is when the amp is trying to produce a slope which is too high, higher than the rate of change the op-amp can support. (The higher the amplitude and/or frequency of the output, the more likely this is to occur.) Thus it will produce a lower slope, which may result in having a sine wave turned into a triangle wave.**

2. (2 points) Look through the textbook chapter on op-amps, and write the names of as many different types of circuits/amplifiers/signal-processors built from op-amps as you can. (Hint: Look at the figures!)

3. Regarding the schematic of the op-amp circuit to the right...

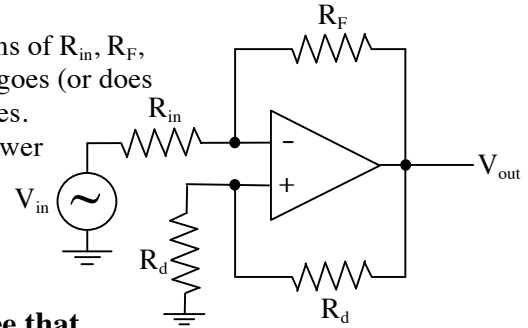- a) Find  $V_+$  and  $V_-$ , the voltages at the + and - inputs, respectively, in terms of  $R_{in}$ ,  $R_F$ ,  $V_{in}$  and  $V_{out}$ . Hint: assume you *know*  $V_{out}$ , think about where the current goes (or does not go), and thus what *simple circuit* each "channel" of the op-amp makes.
- b) If the  $R_F$  feedback loop functions so as to force  $V_+ = V_-$ , use your answer to part (b) to compute the gain of the amplifier (in terms of  $R_{in}$  and  $R_F$ ).
- c) Is this amplifier inverting or non-inverting?



**Answer:**

**3. a) Treating each current path as a "voltage divider," we see that**

$$V_+ = V_{out} \frac{R_d}{2R_d} = \boxed{\frac{V_{out}}{2}},$$

$$V_- = V_{in} + (V_{out} - V_{in}) \frac{R_{in}}{R_{in} + R_F}.$$

*In greater detail: If we say the current flows from  $V_{in}$  to  $V_{out}$ , we can follow the voltage changes as follows:*

$$V_{in} - IR_{in} - IR_F = V_{out},$$

*from which we find the current*

$$I = \frac{V_{in} - V_{out}}{R_T},$$

*where  $R_T = R_{in} + R_F$ . (Note: The choice of direction of current flow is arbitrary; we could just as easily reverse the direction and the sign of current.) The voltage  $V_-$  is found by either following the voltage changes "down" from  $V_{in}$  or "up" from  $V_{out}$ :*

$$V_- = V_{in} - IR_{in} \quad (\text{also} = V_{out} + IR_F).$$

*...Substituting in for  $I$  yields the full expression for  $V_-$ .*

**b) Setting  $V_+ = V_-$ , we find**

$$\frac{V_{out}}{2} = V_{in} + (V_{out} - V_{in}) \frac{R_{in}}{R_T}.$$

**Collecting like terms gives**

$$V_{out} \left( \frac{1}{2} - \frac{R_{in}}{R_T} \right) = V_{in} \left( 1 - \frac{R_{in}}{R_T} \right),$$

**from which we find the total gain**

$$G = \frac{V_{out}}{V_{in}} = \frac{\left( 1 - \frac{R_{in}}{R_T} \right)}{\left( \frac{1}{2} - \frac{R_{in}}{R_T} \right)} = \frac{\left( \frac{R_F}{R_T} \right)}{\left( \frac{1}{2} - \frac{R_{in}}{R_T} \right)} = \frac{R_F}{\frac{1}{2}(R_F - R_{in})} = \boxed{\frac{2}{1 - R_{in}/R_F}}.$$

c) Looking at the expression for gain  $G$ , we see that...

for  $R_{in} < R_F$ , the gain is *positive* and the amp is *non-inverting*, but...

for  $R_{in} > R_F$  the gain is *negative* and the amp is *inverting*.

The case of  $R_{in} = R_F$  produces a gain which is *indeterminate*.

4. Problem 33-28

**They are in phase. The amp shown is a non-inverting amplifier.**

5. Problem 33-39

**See answers in back of text**

6. Problem 33-50

Since  $V_- = V_+$ , and  $V_+ = 0V$ ,

$V_{out} = I_{in} R$ .

a.  $(.002 A)(1000 \Omega) = 2 V$

b.  $3 V$

c.  $10 V$