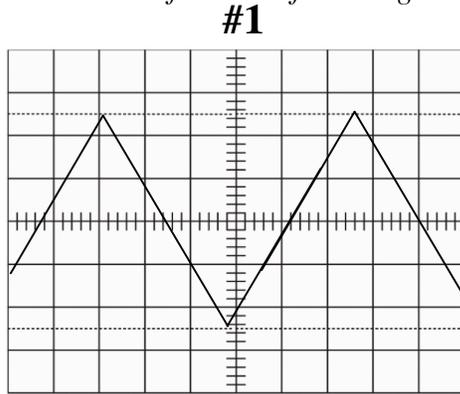



PHY2250 - Electronics & Circuit Theory Practice Test 2

Show all work
 Turn off (OFF) all cell phones
Answer on separate paper. Hand in this sheet separately.
Answers on this sheet will not be considered.
 100 points total

Questions 1 and 2 refer to the following oscilloscope traces:



Volts/div: 0.5V
 Time/div: 20µs

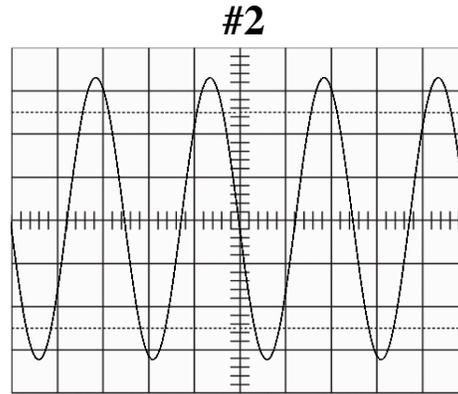

Volts/div: 0.1 mV
 Time/div: 2µs

1. (12 points) Identify each of these characteristics/values for the signal above on the left.
 - a) Type of signal (i.e., the "name" of the "wave shape") **Answer: Triangle wave**
 - b) Amplitude **Answer: $V_{pp} = (5\text{div}) \cdot (0.5\text{V/div}) = 2.5\text{V}$. $A = V_{pp}/2 = 1.25\text{V}$**
 - c) Frequency **Answer: $T = (5.5\text{div}) \cdot (20\mu\text{s/div}) = 110\mu\text{s}$, $f = 1/T = 9.1\text{kHz}$**

2. (12 points) Identify each of these characteristics/values for the signal above on the right.
 - a) Type of signal (i.e., the "name" of the "wave shape") **Answer: Sine wave**
 - b) RMS voltage V_{RMS} **Answer: $(0.32\text{mV}) \cdot (0.707) = 0.23\text{ mV}$**
 - c) Period **Answer: $T = 5.0\ \mu\text{s}$**

Multiple Choice: In the following problems, choose the "best" answer.

3. (5 points) What is the capacitance of a capacitor if it can store 6.0 mC of charge when 78 V is applied across the plates?
 - a) 470 mF
 - b) 77 µF
 - c) 4.7 F
 - d) 82 mF
 - e) None of the above

4. (5 points) An AC current with amplitude 1mA is sent into a "step up" transformer with a turns ratio of 100. The current in the secondary is therefore (ideally)
 - a) 100 mA
 - b) 10 mA
 - c) 0.1 mA
 - d) 10 µA
 - e) None of the above

5. (5 points) The ratio of the charge on a capacitor to its capacitance is equal to the
 - a) current through the capacitor
 - b) voltage across the capacitor
 - c) impedance of the capacitor
 - d) None of the above

6. (5 points) A 50Ω resistor, 10nF capacitor and a 300mH inductor are connected in series and driven with a sine wave at 1kHz . Which component has the greatest impedance?

- a) the resistor b) the capacitor
 c) the inductor d) the source e) Impossible to determine

7. (5 points) Direct current through a wire produces...

- a) no magnetic field. b) an alternating magnetic field.
 c) a constant magnetic field. d) Both (b) and (c).

8. (5 points) In an LR circuit, measuring output voltage across the resistor results in a ____ filter.

- a) low pass b) high pass
 c) bandpass d) short pass

9. (5 points) The region of a PN junction consisting of charged ions is called the...

- a) no-current region. b) reverse breakdown region.
 c) barrier region. d) depletion region.

10. (5 points) The forward voltage drop across a typical LED is around...

- a) 0.7 V . b) 0.3 V .
 c) 10 V . d) 2 V .

11. (5 points) A typical semiconductor has ____ valence electrons.

- a) zero b) two
 c) four d) eight

Short Answer: In the following problems, remember to **show your work** and/or **explain your answer** in completing the calculations. **An answer by itself will not receive credit.**

12. (10 points) The last stage of a power supply for some piece of electronic gear uses a DC source of 8V to charge a capacitor of 11nF in series with a resistor of 2500Ω . How long does it take for the capacitor to reach 63% of the source voltage?

$$V_C = V_{\max} \left(1 - e^{-\frac{t}{RC}} \right)$$


$$\frac{V_C}{V_{\max}} - 1 = -e^{-\frac{t}{RC}}$$

$$\ln \left(1 - \frac{V_C}{V_{\max}} \right) = -\frac{t}{RC}$$

$$t = -RC \ln \left(1 - \frac{V_C}{V_{\max}} \right) = -(2500\Omega)(11 \times 10^{-9}\text{F}) \ln(1 - 0.63)$$

$$t = 27\mu\text{s}$$

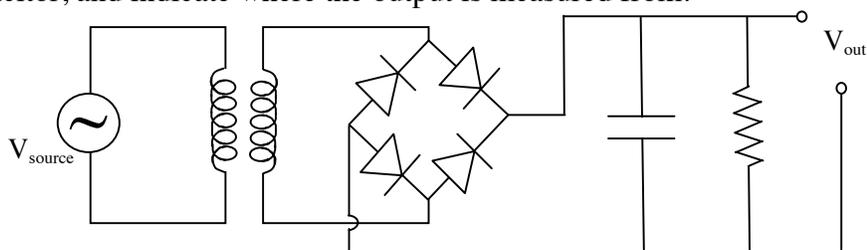13. (11 points) Draw a schematic for a DC power supply, consisting of a transformer, bridge rectifier, resistor and capacitor, and indicate where the output is measured from.



14. (10 points) The capacitors, $C_1=20\mu\text{F}$, $C_2=15\mu\text{F}$, and $C_3=10\mu\text{F}$, are connected in parallel.

a) If this parallel combination is connected to a 10V DC power supply and allowed to fully charge, what is the charge on *each* capacitor?

b) If this parallel capacitor combination is connected in series with a 20Ω resistor to a 100Hz AC source, find the total impedance.

Answer:

a) $Q_1 = VC_1 = (10\text{V})(20\mu\text{F}) = 200\mu\text{C}$

$$Q_2 = VC_2 = (10\text{V})(15\mu\text{F}) = 150\mu\text{C}$$

$$Q_3 = VC_3 = (10\text{V})(10\mu\text{F}) = 100\mu\text{C}$$

b) $C_T = C_1 + C_2 + C_3 = 45\mu\text{F}$

$$X_C = \frac{1}{2\pi f C_T} = \frac{1}{2\pi(100)(45 \times 10^{-6})} = 35.4\Omega$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{20^2 + 35.4^2} = 40.7\Omega$$

Extra Credit:

(5 points) The capacitor in a certain condenser microphone has a variable plate separation. The voltage across the capacitor is kept at a constant 48V by phantom power. If the capacitor in its "default" separation has a capacitance of $30\mu\text{F}$ and then the plate separation *decreases* by a factor of 2 in 2ms, find the current that flows.

$$I = \frac{\Delta Q}{\Delta t} = \frac{\Delta(CV)}{\Delta t} = V \frac{\Delta C}{\Delta t}$$

$$\Delta C = (C_f - C_i), \text{ and } C \propto \frac{1}{d}, \text{ so } C_f = 2C_i = 60\mu\text{F}$$

$$I = 48\text{V} \frac{(60\mu\text{F} - 30\mu\text{F})}{2\text{ms}} = 0.72\text{A}$$