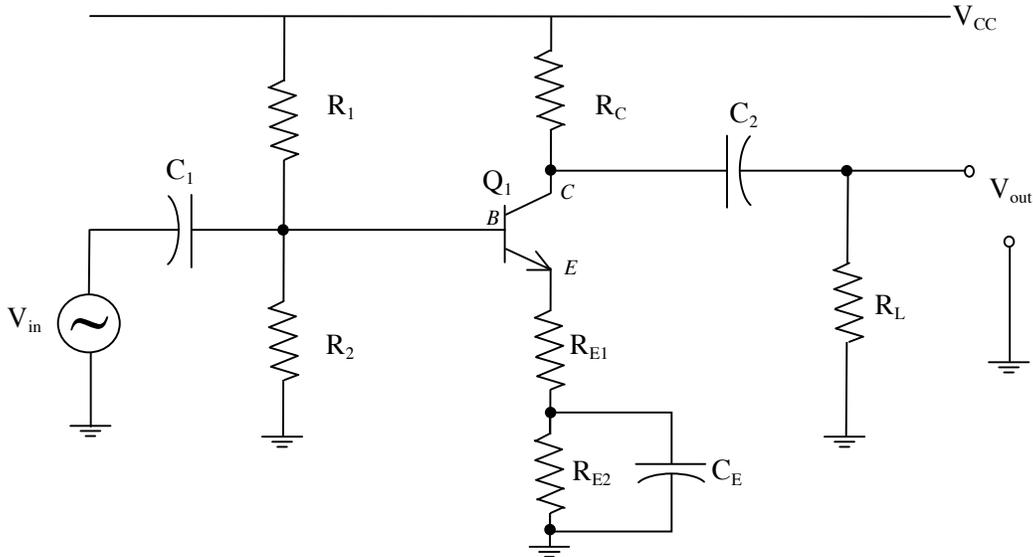



## PHY2250, Dr. Hawley: AC Operation of a Common-Emitter Amplifier

We've previously discussed the DC operation of a common-emitter amplifier, DC load lines, Q points, etc. We now consider the AC operation of such an amplifier. We're going to put two resistors on the emitter, along with a bypass capacitor as shown:



( $R_{E1}$  can either be an explicit resistor or it can represent the effective "resistance" which appears in real-world performance of diodes, i.e. the fact that there is a finite slope to the line on current-vs.-voltage graph for a diode, rather than an "instant" transition at 0.7V.)

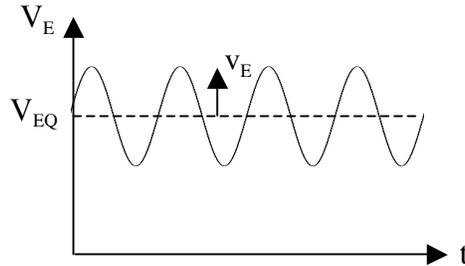Let's break all quantities into their DC and AC parts, which will be denoted by a subscript "Q" and a lower-case letter, respectively. So, e.g.,  $V_E = V_{EQ} + v_E$ , as shown in the following graph:



Note that because of the "diode drop" between the base and the emitter,  $V_E = V_B + 0.7V$ . The "AC part" of this equation tells us that  $v_E = v_B$ . A simple proof follows:

$$\begin{aligned} V_E &= V_B - 0.7V \\ V_{EQ} + v_E &= V_{BQ} + v_B - 0.7V \\ V_{EQ} + v_E &= (V_{EQ} + 0.7V) + v_B - 0.7V \\ v_E &= v_B. \end{aligned} \tag{1}$$

Because of bypass capacitor  $C_E$  allows AC signals to go "around"  $R_{E2}$ , the AC part of the emitter voltage,  $v_E$ , is given by

$$v_E = i_E R_{E1}. \tag{2}$$

The collector voltage,  $V_C$ , is given by

$$V_C = V_{CC} - I_C R_C$$

$$V_{CQ} + v_C = V_{CC} - (I_{CQ} + i_C)R_C,$$

and the "AC part" of this means that

$$v_C = -i_C R_C. \quad (3)$$

We are now ready to compute the voltage gain of this amplifier.

The **AC Voltage Gain**  $A_V$  is defined to be the ratio of the AC parts of output voltage to input voltage,

$$A_V = v_{out} / v_{in}.$$

Considering that  $v_{in} = v_B = v_E$ , and  $v_{out} = v_C$ , we find

$$A_V = v_C / v_E = -i_C R_C / i_E R_{E1}.$$

Given that the AC beta  $\beta \equiv i_C / i_B$  is a large number (close to the value of  $\beta_{DC} \equiv I_C / I_B$ , which is on the order of 100),  $i_C$  and  $i_E$  are approximately equal. Therefore the gain of the amplifier is

$$A_V = -\frac{R_C}{R_{E1}}.$$

So by lowering the value of  $R_{E1}$ , we can increase the gain of the amplifier.

What then is the function of the resistor  $R_{E2}$ ? It affects the DC operation of the amplifier, i.e. it controls the placement of the Q point on the DC load line. Recall that

$I_{EQ} = V_{EQ} / (R_{E1} + R_{E2})$ , and since  $I_E$  is approximately equal to  $I_C$ ,

$$\begin{aligned} V_C &= V_{CC} - I_C R_C \\ &= V_{CC} - V_{EQ} R_C / (R_{E1} + R_{E2}). \end{aligned}$$

So the combination  $R_{E1} + R_{E2}$  takes the place of the single  $R_E$  in our previous studies of the DC characteristics of the amplifier.