

Scott H. Hawley, Ph.D.
Chemistry & Physics Dept.
Belmont University
Nashville TN

*To the Electronics & Circuit Theory students, past and present:
Thanks for your flexibility, ingenuity,
and senses of humor.*

*And to Sal:
Thanks for all your advice and help, man.*

Table of Contents

Welcome and Orientation	5
Rules of the Physics Lab	6
Reference: Guidelines & Troubleshooting	7
Lab: Ohm's Law	8
Reference: Resistor Color Code	13
Lab: Resistivity of Conductors	14
Lab: Internal Resistance	20
Pre-Lab: Breadboarding & Loaded Voltage Divider	22
Lab: Breadboarding & Loaded Voltage Divider	23
Pre-Lab: Oscilloscope Orientation	26
Lab: Oscilloscope Orientation	27
Lab: RC Circuits	30
Lab: Loudspeaker Impedance	33
Lab: Transformers	34
Lab : Diodes & DC Power Supplies.....	38
Lab: Transistors & Simple Amplifier.....	41
Pre-Lab: Op-Amps	44
Lab: Op Amp Circuits	46
Lab: Distortion!	49
Reference: Formulas & Prefixes	50
Student's Notes:	51

Welcome and Orientation

You have in your hands the most advanced, most up-to-date laboratory manual for Physics 2250 at Belmont University ever devised by man. The material in this book is constantly being refined to make the laboratory component of the course more fruitful. Countless circuit components have been burned out by *real live students* in testing the labs contained herein, to bring you the very best.

This course provides a survey of basic analog electronics. Students in Physics and Computer science will benefit greatly for this course, although it is primarily geared toward Audio Engineering Technology (AET) majors. The course itself is a co-requisite for Sal Greco's Studio Maintenance I class, in which students apply the concepts they learn in Physics 2250 to electronics work in recording studios.

The importance of hands-on experience with circuits cannot be overestimated. Simply learning the "theory" behind circuitry is very different from having to apply that knowledge in the real world. This is why the laboratory component of the course is essential: *Always come to lab, and always bring your lab book!*

Here are a few of the things we will be doing in lab:

- Designing and building circuits
- Troubleshooting
- Using measurement devices (e.g., oscilloscopes)
- Building "signal processors" such as filters & amplifiers
- Transforming our "book knowledge" into practical knowledge

Here are a few things we will *not* be doing in lab:

- Soldering - because of space & safety concerns. Twenty students in close quarters all with burning hot, pointy irons in hand is not something we're able to safely accommodate. Instead we'll build our more complicated circuits using solderless breadboards.
- Wire-stripping - because we don't have to. The solderless breadboards we use accommodate pre-stripped jumpers which we have in kits, in order to maximize our time and avoid the tedium of stripping wires.
- Building our own audio gear. The level, pacing and size of this class do not easily accommodate individual projects. The choice has been made that all students will complete the same lab assignments, and to allow project-building to occur primarily the Studio Maintenance I & II classes.

Rules of the Physics Lab

Be aware that the rules of the lab are for your safety and the safety of others. These rules are based on the guidelines set forth by the EPA and OSHA. Failure to abide by these rules violates Belmont, EPA and OSHA policies.

1. Always use appropriate safety equipment as designated by the lab instructor.
2. Always wear appropriate clothing, including closed-toe shoes. NO sandals, flip flops, etc are permitted. "No shoes, (no shirt,) no service."
3. Long hair must be restrained.
4. Book packs, bags, purses, coats, etc. must not obstruct walkways.
5. ABSOLUTELY NO food or drink in the lab. This includes food, water bottles or drinks in book bags, purses, coats, etc.
6. Follow all the instructions of the instructor and/or assistant.
7. Report any accidents or spills to the instructor.
8. You may only work in the lab during your assigned lab time. Make-up labs may be arranged at the discretion of the instructor in the event of an excused absence.
9. Your work area and common areas must be clean before you leave the lab.
10. All waste must be discarded in appropriate container.
11. Know the locations of all exits, fire extinguishers, fire blankets, eyewashes, and safety showers.

Reference: Guidelines & Troubleshooting

Here is a quick-reference guide for methods used in the laboratory.

General Guidelines:

- When using measurement equipment (e.g., multimeters, oscilloscope) Always use the scale which gives you the greatest level of precision possible. This typically means the *lowest* setting (e.g. 200mV) for which you can still get a reading.
- Ammeters go in *series*. Never parallel.
- Pay attention to where the oscilloscope ground clip is placed.

Troubleshooting Ideas:

- Trace the "signal path": Start from the + output on the source, and follow the current all the way back to the "-" (or "GND") terminal on the source.
- Test each part of the circuit independently.
- Burned-out components and damaged wires will often become "open".
- Test for open circuit (components) using an Ohmmeter. Open circuits will show an infinite resistance ("1" or "OL" on all scales of Ohmmeter)
- Ammeters may be faulty due to a blown fuse. Try a different meter.
- Breadboard holes are very small. Make sure that components you want to be connected really *are* connected via your using of breadboard columns.
- When you can't see any oscilloscope trace at all, switch the channel's voltage switch to "GND", make sure the intensity is up, and turn the "Vert. Pos." knob until you see the green line. Then switch from "GND" to "AC" or "DC", as appropriate.
- If all you're able to see on the 'scope is a flat green line, make sure the channel's voltage switch is no longer set to "GND", increase the setting of "Sec./Div.", decrease the setting of "Volts/Div.", and make sure you're both triggering on ("Source") and displaying ("Mode") the channel you have connected to the circuit.

Lab: Ohm's Law

Purposes:

To explore the relation(s) between voltage, current and resistance in a circuit. To learn how to construct simple circuits. To gain familiarity in using equipment such as a DC power supplies and multimeters.

Equipment:

- 1 DC power supply
- 2 Multimeters (without leads)
- 5 Wires with banana ends (2 black, 2 red, 1 other color)
- 2 Banana-alligator clips (with rubber shielding)
- Your textbook
- 2 Resistors with different color codes (e.g., 500Ω and $100k\Omega$)
- Computer (e.g., laptops shared between students)

Important Safety notes:

While every reasonable precaution has been taken to ensure your safety during this lab, when working with electric circuits there is always the "potential" for accidental shock and/or injury. The following guidelines will help to make for a safe and enjoyable lab experience:

- Don't *ever* put your finger on a resistor "to see if it's hot". If it *is* hot, you'll burn yourself. Resistors never "look" hot, so just don't touch one when it's in a circuit. In fact...
- Don't touch *any* part of the circuit while the current's flowing or when the DC power supply is on. You may think it's safe and you know what you're doing... Assume it's *not* safe and you *could* have made a mistake. Turn the power off first.
- Never exceed the *maximum wattage rating* for the resistor. You can burn it out and even damage other equipment
- When the multimeter is in ammeter mode, it goes in *series*. Series, series, series. Not parallel. Never parallel. You can really break things if you put the ammeter in parallel.

On a separate sheet, you will attest in writing to that you've read these guidelines.

Use of Meters:


We'll be using digital multimeters to measure Ohms, Volts and (milli or mico) Amps. Although our DC power supplies have their own indicators of current & voltage, we'll use our own meters because they offer greater precision. When making a measurement with a meter, start on the largest range possible (exception: for some current measurements, the "10A" input is unfused -- use the "200mA" as shown later on in this lab description), and turn the range down until you can read as many significant digits as possible without exceeding the maximum range for the setting you're using. In general, *avoid* flipping the dial on the meter around while the current is flowing.

Procedure:


You'll repeat the following steps for **two** resistors.

1. Read the color code for the resistor. If you need to, refer to the color code guide in the textbook. Write the colors and the value on the data sheet provided.
2. Using an Ohmmeter (as described in the text), measure the resistance of the resistor. Write the value in the appropriate place.
3. Using the value of R obtained from the Ohmmeter, calculate the *maximum voltage* you can safely apply across the resistor and not exceed the 1/2 watt rating of the resistor. Write this value on the data sheet.
4. Next you'll measure current vs. voltage through the resistor via the following steps:
 - a. Set up a circuit as shown in the diagram(s) below. Don't turn the power on yet!

Schematic diagram:

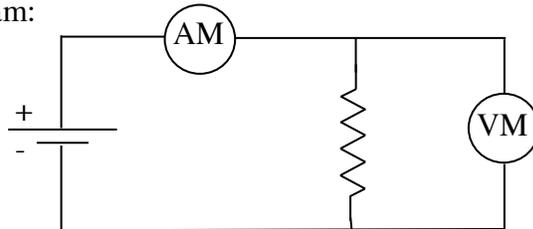

"Physical" diagram (not to scale!):

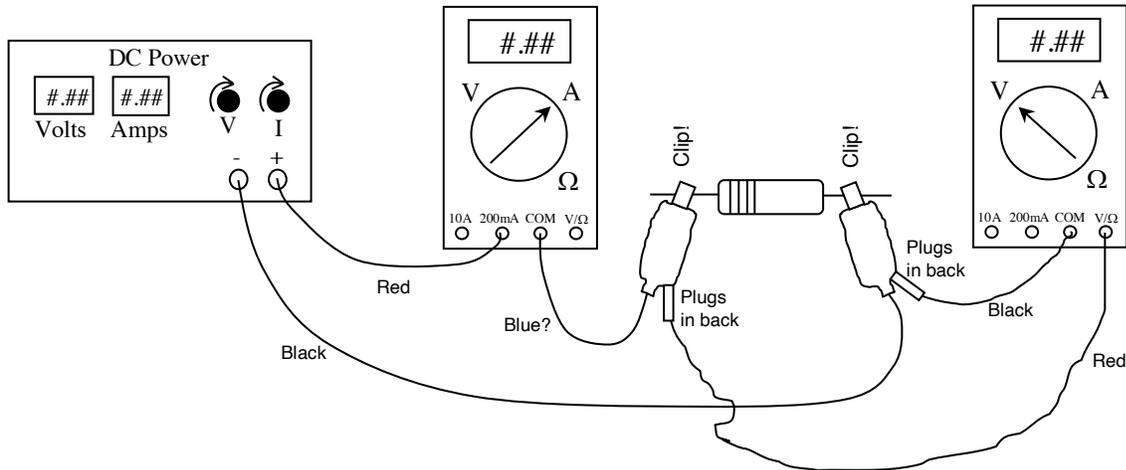


- b. Make sure the voltage and current knobs on the power supply are turned all the way counter-clockwise (zero voltage and current).
- c. To avoid overloading the meters: Make sure the ammeter (multimeter set to "A") is on the maximum range for the 200mA setting, and the voltmeter (multimeter set to "V") is on the 200V range. Once the power is on, you may safely decrease the maximum range setting as needed.
- d. Now you should be ready to go. Flip the power on the DC power supply and turn the current knob up about halfway. (If the current knob is not turned up high enough for a given voltage, you may end up "current limited".)

- e. Measure current *through* and voltage *across* the resistor for at least six values of voltage (never exceeding the maximum voltage). Write these in the spaces provided, being sure to keep track of the *units* (e.g. mA or μA).
 - f. Enter these values in an Excel Spreadsheet, and calculate the values of V/I for each pair of values. Also make an "XY Scatter" plot of V vs. I for these values.
 - g. Fit a line to your data: Right click on a data point, and select "Add Trendline" on the pop-up menu. Select "Linear" and under "Options", tell Excel to print the slope and intercept on the graph, as shown in the example graph (below). The *slope* of this trendline (the number before the "x") constitutes *another* measure of resistance.
 - h. Print out the graph (the printer is in HSB101)
5. Answer the questions on the following page.
 6. Staple together your data sheet, answered questions, and graph printout(s) and turn them in. You're finished!

Sample Data for Ohm's Law Lab


Resistor 1 (R,R,R,Gold)
 R from color code (Ω): 2200
 Min R (w/in 5% Tolerance): 2090
 Max R (w/in 5% Tolerance): 2310
 Ohmmeter (Ω): 2200
 Max V for 0.5W: 33.16625

I (mA)	I (A)	V (V)	V/I (Ω)
0.409	0.000409	0.863	2110.024
1.065	0.001065	2.22	2084.507
1.56	0.00156	3.04	1948.718
3.18	0.00318	5.91	1858.491
4.83	0.00483	9.28	1921.325
5.99	0.00599	11.46	1913.189

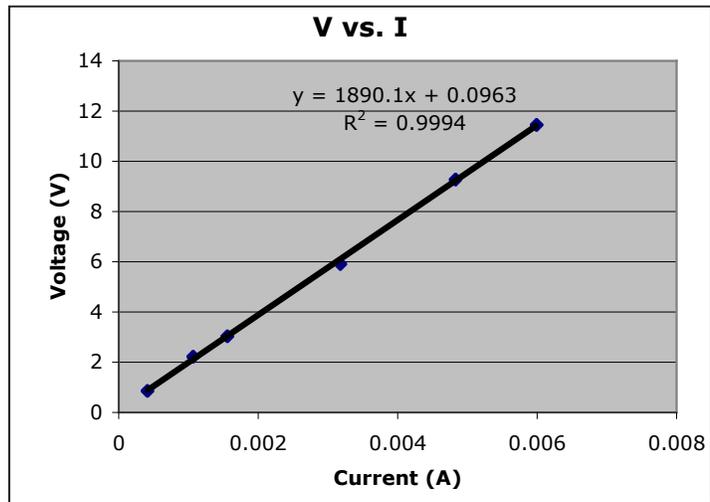

Resistor 2 (Y,Blue,Y,Gold)
 R from color code (Ω): 4.70E+05
 Min R (w/in 5% Tolerance): 4.47E+05
 Max R (w/in 5% Tolerance): 4.94E+05
 Ohmmeter (Ω): 4.74E+05
 Max V for 0.5W: 484.768

I (μA)	I (A)	V (V)	V/I (Ω)
2.5	2.5E-06	0.972	388800
8.9	8.9E-06	3.44	386516.9
23	0.000023	8.86	385217.4
36.4	3.64E-05	14.04	385714.3
69.1	6.91E-05	26.5	383502.2

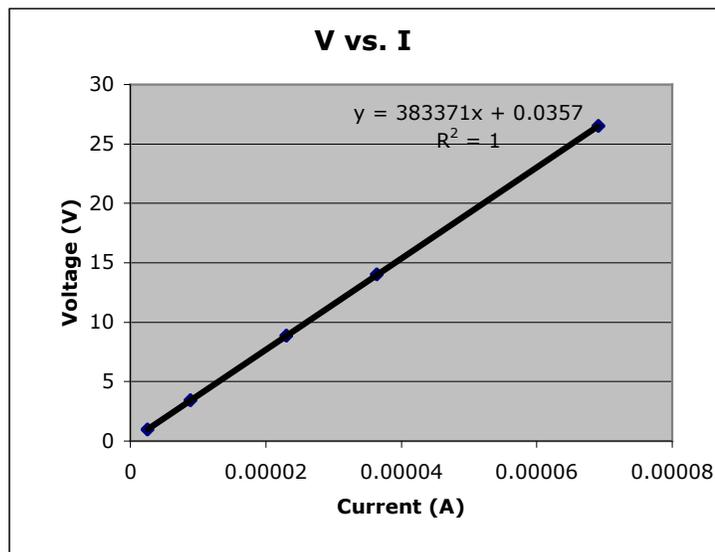

Ohm's Law Data Sheet **Name(s)** _____

Resistor 1:

Color Code: _____ _____ _____ _____

R from Color Code: _____ +/- _____ R from Ohmmeter: _____

Maximum Voltage for 0.5W: _____

Voltage (units?)	Current (units?)

Resistor 2:

Color Code: _____ _____ _____ _____

R from Color Code: _____ +/- _____ R from Ohmmeter: _____


Maximum Voltage for 0.5W: _____

Voltage (units?)	Current (units?)

Questions: Answer these as they apply to *both* resistors you measured.

1. How do your different determinations of resistance (color code, ohmmeter, V vs. I) agree or disagree?
2. Are the measurements within the tolerance value for the resistor(s)?
3. To what extent is Ohm's Law being obeyed or not? (e.g., is the graph of V vs. I at least *linear*?)
4. Do you notice any trends in the V/I ratio as you change the voltage? If so, what are they?
5. What might be responsible for the difference(s) in the resistance values you measured/calculated?
6. Which method for measuring resistance do you regard to be the most accurate? Why? Which is the least accurate and why?
7. Given these differences in resistance values, how would apply this knowledge when it comes time to design your own electronic circuitry?

Reference: Resistor Color Code

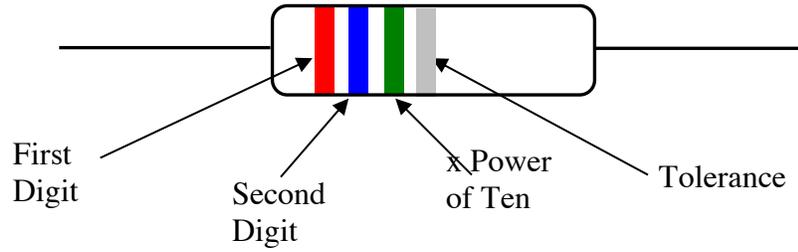

Colors:	Digit	Mnemonic (Make your Own)
Black	0	B_____
Brown	1	B_____
Red	2	R_____
Orange	3	O_____
Yellow	4	Y_____
Green	5	G_____
Blue	6	B_____
Violet	7	V_____
Gray	8	G_____
White	9	W_____
Tolerances:		
Gold	+/- 5%	
Silver	+/- 10%	
None	+/- 20%	

Example:

A resistor with bands Red, Blue, Green, Silver.

Red	Blue	Green	Silver
2	6	5	10%

$$= 26 \times 10^5 \pm 10\% = 2.6 \times 10^6 \pm 2.6 \times 10^5 = 2.6 \pm 0.26 \text{ M}\Omega.$$

Lab: Resistivity of Conductors - *NOTE: Usually we skip this lab, and go on to Internal Resistance*

Purpose: To investigate the effects of wire length, cross-sectional area and Resistivity on the resistance of conductors

Equipment:

- DC power supply, with a readout for current in Amperes
- PASCO EM-8812 Resistivity Apparatus, and Wire Set
- 1 DC Voltmeter
- 4 Wires with banana ends
- Your textbook: Electronics: A Complete Course by Nigel P. Cook
- Computer (e.g., laptops shared between students)

Introduction:


Recall that the functional dependence of resistance R on length ℓ , cross-sectional area A and resistivity ρ is (supposedly) given by

$$R = \rho \frac{\ell}{A}.$$

The Apparatus:

It has current-limiting resistors in it, and a **2 Amp fuse**. You do not want to blow this fuse! The current-limiting resistors mean that the resistance of the wire sample will have only a small effect on the current in the (series) circuit. In fact, each wire sample will only acquire tens of millivolts and have a resistance of tenths of an Ohm.

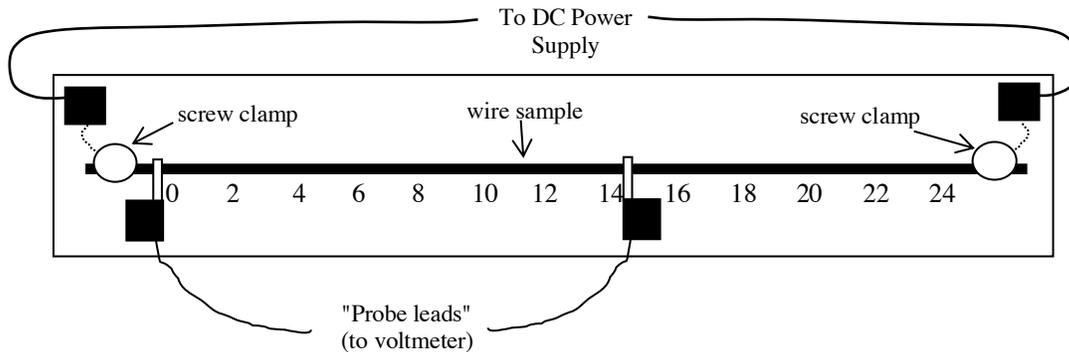Below is a picture of the apparatus. *You should NOT connect it until instructed to do so in the Procedure, below.*



Procedure:

This lab will be conducted in three successive parts:

Part I: Variation of Resistance with Length

1. Choose the copper conductor with diameter $D = 0.040$ inches, which equals 40 mils. (1 mil = 1 thousandth of an inch). Attach it to the Resistivity Apparatus in the following way:
 - a. Push the two "probe leads" all the way to the "outside" of the apparatus.
 - b. Thread the copper wire *under* the probe leads and into the metal clamps at the sides of the apparatus.

- c. Screw the clamps down so that electrical contact is made. Note that power from the power supply will make *direct contact* with these clamps.
2. Hook up the leads of the voltmeter to the two probe leads, and use the "200mV" setting.
3. With the DC power supply off, connect the positive and negative terminals to the other banana ports on the sides of the apparatus.
4. On the power supply, turn the voltage knob and the current knob all the way down, and flip on the power switch for the supply.
5. We want to make sure we stay well below the 2A limit on the Resistivity Apparatus. So adjust the voltage and current knob so that the readout on the power supply reads **1.5 Amperes**. You can now leave the power supply at these settings for the *entire* lab. There is no need to adjust the power supply settings in the exercises that follow.
6. Now set the left probe lead at zero centimeters. By placing the right probe lead at different locations spaced out along the length of the conductor, take six voltage readings from the voltmeter. (We recommend 2cm, 4cm, 8cm, 14cm, 19cm and 24cm, but you may use other values.) These will likely range from 0.5 mV to 8mV.
7. Using the current of 1.5A and Ohm's Law, convert your voltage readings into resistance values.
8. Make a plot of resistance R vs. the length ℓ of the conductor. You may want to express the resistance in Ohms and the length in feet (1 inch = 2.54 cm, 1 foot = 12 inches) before making the chart.
9. Fit a trendline to this, and for "Options," select "Set intercept $y = 0$ " and "Display Equation on Chart".
10. The slope of this line gives you a measure of R/ℓ , which you can then multiply by the cross sectional area $A = (40 \text{ mil})^2 = 1600 \text{ cmil}$, to get the resistivity ρ .

Part II: Variation of Resistance with Area

1. Disconnect the power supply. Now slide the probe leads to the far sides of the apparatus, unscrew the clamps and remove the copper.
2. Select the thinnest brass wire ($D = .020 \text{ in} = 20 \text{ mil}$) and attach it as you had the copper. Reconnect the power supply, and note that the current reading on the power supply is probably no longer 1.5A. This is to be expected. Just make a record of the current value every time you switch the wire sample, but do not adjust the power supply.
3. Set the probe leads to "0 cm" and "24 cm", and measure the voltage across the wire.
4. Repeat 1-3 with the other three gauges of brass wire, making sure to record the current from the power supply each time. Use the *same* length of wire for *each* sample.
5. Noting that cross-sectional area in "cmil" is simply the square of diameter in mils, compute the reciprocal of the area, $1/A$, for each of these wire gauges.
6. Using your voltage and current readings, compute resistance values for each brass wire.
7. Make a plot of R vs. $1/A$, and fit a line to it.
8. Similarly, you can take the slope of this line, divide by the length of the wire ℓ , and find the resistivity ρ .

Part III: Variation of Resistivity with Material

Repeat the method for Part I, using aluminum and nichrome wires as well, i.e. plot resistance vs. length for each of these. *Remember to have the power supply disconnected when attaching the wires and screw clamps!* Calculate resistivities for both materials.

Conclusions: Answer the questions which follow the data sheet.


Sample Data:

Part I: R vs. L for Copper

Current (A) = 1.5

L (cm)	V (mV)	L (ft)	R (Ohms)
2	0.6	0.06562	0.0004
4	1.3	0.13123	0.00086667
8	2.6	0.26247	0.00173333
14	4.5	0.45932	0.003
19	6.1	0.62336	0.00406667
24	7.8	0.7874	0.0052

Slope (Ohm/ft) = 0.00657
 D (mil) = 40
 A (cmil) = 1600
rho (Ohm cmil/ft) 10.5

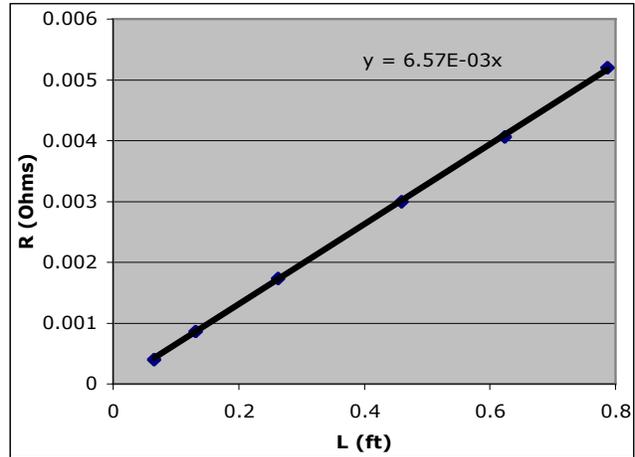


Part II: R vs. 1/A for Brass

Length (cm) = 24

D (mil)	I (A)	V (mV)	1/A (1/cmil)	R (Ohms)
20	1.31	115.7	0.0025	0.088321
32	1.44	47.4	0.00097656	0.032917
40	1.45	30.8	0.000625	0.021241
50	1.45	20.3	0.0004	0.014

Slope (Ohm*cmil) = 35.054
 Length (ft) = 0.78740157
rho (Ohm cmil/ft) 44.5

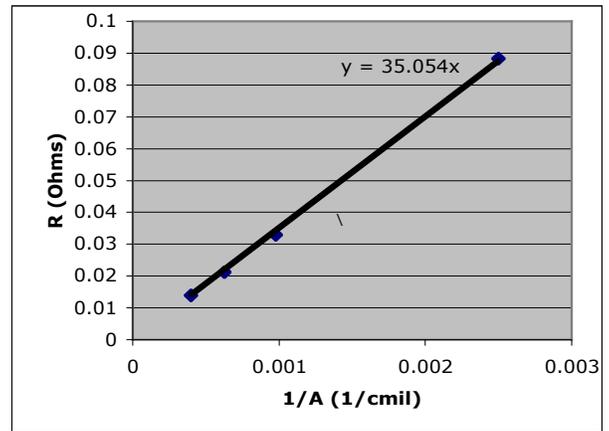

Part III: R vs. L for Aluminum & Nichrome, D=40 mil

Aluminum:

Current (A) = 1.45

L (cm)	V (mV)	L (ft)	R (Ohms)
2	1.7	0.06562	0.00113333
4	3.5	0.13123	0.00233333
8	7	0.26247	0.00466667
14	12.2	0.45932	0.00813333
19	16.6	0.62336	0.01106667
24	21	0.7874	0.014


Slope (Ohm/ft) = 0.0178
rho (Ohm cmil/ft) 28.5

Nichrome:

Current (A) = 1.04

L (cm)	V (mV)	L (ft)	R (Ohms)
2	20.9	0.06562	0.01393333
4	41.5	0.13123	0.02766667
8	82.2	0.26247	0.0548
14	143.4	0.45932	0.0956
19	194.8	0.62336	0.12986667
24	246	0.7874	0.164

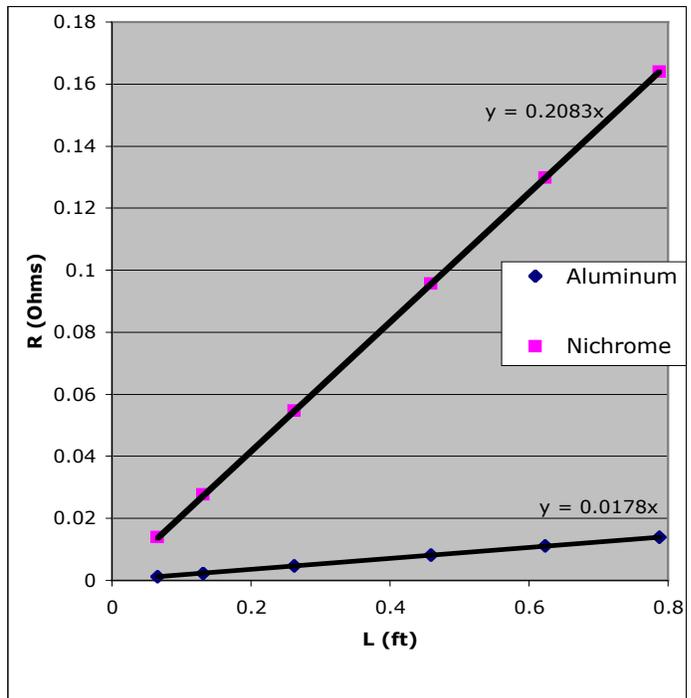Slope (Ohm/ft) = 0.2083
rho (Ohm cmil/ft) 333



Resistivity Data Sheet Name(s) _____
 (You may record values directly to a spreadsheet if you wish, provided it is will-annotated.)

Part I: Resistance vs. Length (Copper)

Current = _____.

Position	Voltage

Slope from line fit = _____ (units?)

Cross-Sectional Area = _____ cmil

Resistivity of Copper (measured) ρ = _____

Part II: Resistance vs. 1/Area (Brass)

Diameter	Current	Voltage

Slope from line fit = _____ (units?)

Length of Wire = _____ inches

Resistivity of Brass (measured) ρ = _____

Part III: Resistivity vs. Material

Repeat resistance vs. length measurements as in Part I, and find resistivities for:

Aluminum, D = 40mil: ρ = _____

Nichrome, D = 40mil: ρ = _____.

Questions:

1. Was R vs. ℓ linear?
2. What about R vs. $1/A$?
3. In what sense was the equation $R = \rho\ell/A$ confirmed or disproved?
4. Compare the resistivity values you measured with those listed in your textbook. How well do they agree or disagree? Be specific.
5. Anything suggestions that would make this lab more interesting and/or "relevant"?

Lab: Internal Resistance

Purposes:


- To gain some experience with series circuits
- To demonstrate that "real world" components, while not perfect, at least have measurable deficiencies

Equipment:

- 1 Voltmeter
- 1 Ammeter
- One voltage source, e.g. "D" Dry Cell Battery
- Variety of resistors, e.g. a resistor bank

Introduction:

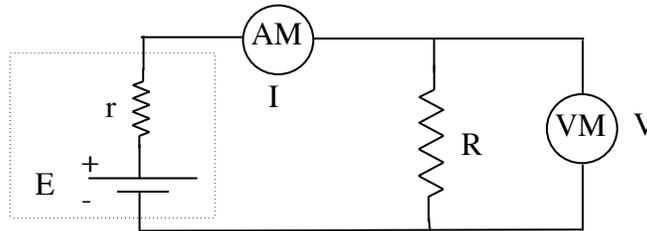The setup will be essentially the same as the Ohm's Law lab, however we will use a battery instead of a DC power supply. The EMF (voltage) of the battery will be represented by E , and its internal resistance r , in the circuit below:



We will neglect the small amount of current which flows through the voltmeter, and the small resistance of the ammeter.

One of the important concepts in series or parallel circuit analysis is *Kirchoff's Loop Rule*: The sum of the voltage changes around any closed loop (in a circuit) is zero. If we regard voltage sources as positive changes in voltage, and resistors and negative changes (of amount $-IR$), then, starting in the lower left corner of the circuit diagram, the sum of the voltage changes around the loop containing the load resistor can be written as

$$E - Ir - IR = 0.$$

But IR is the same as the potential difference measured across the load resistor, V . Thus we can rearrange the above expression as

$$V = -rI + E.$$

Note that this has the form of a linear equation, $y = mx + b$.

Procedure:

1. Set up the circuit in a similar manner to that of the Ohm's Law lab.
2. Vary the load resistance R in the circuit (you do not need to record the resistances) and record various readings of the current I and the potential difference across the load resistor, V .
3. Make a graph of V vs. I (i.e. voltage on the y axis, current on the x axis).
4. Fit a line to the graph, and record the slope and y -intercept of this line. These tell you the "ideal" EMF of the battery, E , and the internal resistance of the battery, r !
5. Print out the graph, answer the questions on the data sheet.

Internal Resistance Lab
Data Sheet

Name(s): _____

Current Reading (units?)	Voltage Reading (units?)

Slope of graph (units?): _____ y-intercept (units?): _____

Questions:

1. What is the internal resistance of your battery?
2. What is E , the "ideal" EMF of the battery?
3. Given these two quantities, what is the theoretical maximum current that could be supplied by the battery? (Consider a short circuit connecting the two ends of the battery.)
4. What is the maximum power that can be delivered by the battery? ($P_{max} = E^2/(4r)$).
5. How does the internal resistance affect the voltage produced by the real battery as a source produces more current? Why does a new 1.5 volt AA battery yield a reading of about 1.60 Volts when not in a circuit?

Lab: Breadboarding & Loaded Voltage Divider

Purpose(s):

- To gain practical experience designing, building and testing series-parallel circuits.
- To see how "load" can affect the performance of a circuit
- To gain familiarity and facility with circuit construction using solderless prototyping boards, i.e. "breadboards"


Equipment:

- Solderless Breadboard
- Wires & Alligator Clips
- Regulated DC power supply
- Assortment of resistors of various values
- Multimeter(s)

Introduction:

For the remainder of this course, we will build our circuits using solderless "protoboards" or "prototyping boards," typically called "breadboards."

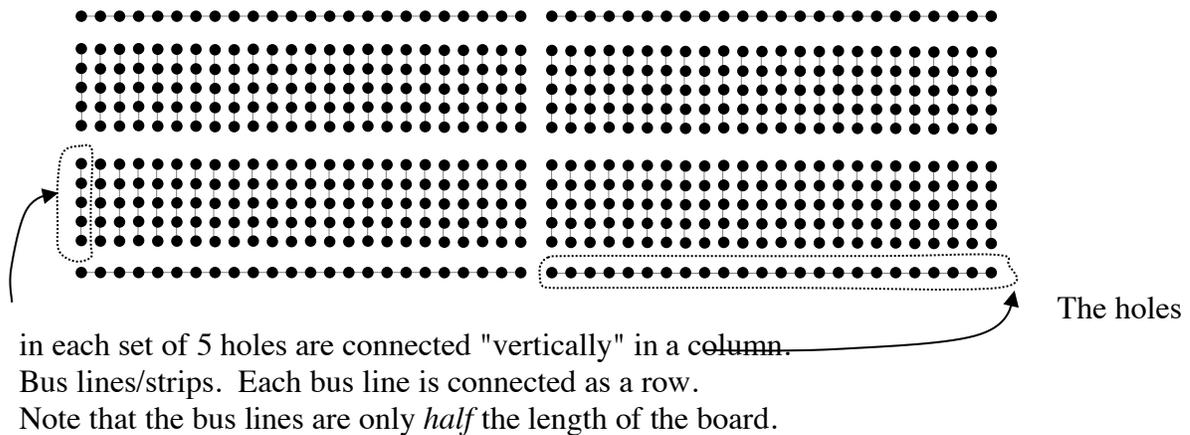The holes in the breadboard are connected in short columns or long rows by conducting strips beneath the board:



Breadboard Etiquette

Convention has it to use the bus lines chiefly for **power distribution**, i.e. connect the + terminal of the power supply to the top bus line, and the - terminal to the bottom bus line.

Components are connected by using holes sharing the same column, and/or via the use of (ideally short) wires called **jumper**s.

The **efficient** and **neat** physical layout of circuit elements is essential to building intelligible and troubleshoot-able electronic circuitry. Refer to pp. 45-47 of the text for such examples. Long wires are to be avoided, because they make for "spaghetti" circuits, making it hard to visually follow signal flow.

The use of **colored jumper wires** is **encouraged**, in order to "label" certain functions (e.g., red for positive, black for negative), and/or to visually group common elements of a circuit together.


Also, it is best to avoid "crossing" jumper wires and/or components whenever possible, again because crossing inhibits easy visual comprehension of current flow.

Jumpers are typically used such that they are flat (or nearly flat) against the breadboard whenever possible. Also, it is good to add "jumpers with one end free" to make it easy to connect/disconnect peripherals such as power supplies and meters (via clipping them to the free end of the jumper wire), that circuit components are not subjected to undue mechanical stress.

There is not a hard line of "right" and "wrong" when building a circuit with a breadboard, however the goal should be to **maximize visual clarity** so that an **outside observer** can easily and quickly determine your circuit layout and follow the path(s) of current.

The Voltage Divider

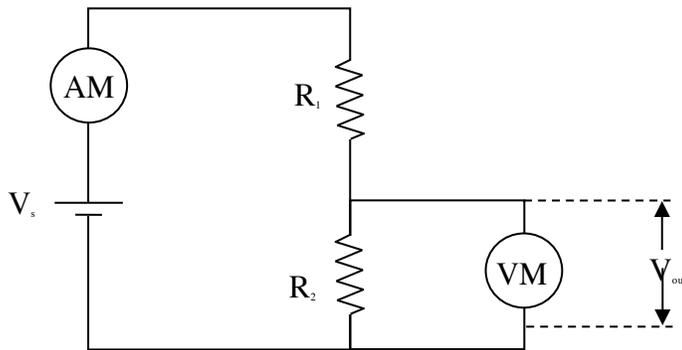In this lab we will study the behavior of a voltage divider circuit under different loads. The circuit shown below is a prototypical voltage divider.



Procedure:

1. Designing the Circuit: Set $V_s = 10V$. Select a resistor for R_1 which is at least as large as the value you found in the prelab. Select a resistor for R_2 which will place V_{out} between 3.5V and 4V. Measure these resistors *with an ohmmeter*, and calculate the expected value of V_{out} . Show your calculations below:

$R_1 =$ _____ $R_2 =$ _____

Expected $V_{out} =$ _____

2. Measurement. Build the circuit shown above and measure the voltage and current through the circuit:

$V_{out} =$ _____

$I_1 =$ _____

3. Loading the divider. Now you will place third resistor, R_3 , in parallel with R_2 , and measure the current I and voltage V_{out} . Do this for five values of R_3 (measured with an ohmmeter!), e.g. $10k\Omega$ down to 100Ω and record the results below.

R_3	V_{out}	I_r

4. Analysis: Make two plots, one of V_{out} vs. R_3 and another of I vs. R_3 .

Conclusions:

1. How did your expected V_{out} agree or disagree with the value of V_{out} you measured for the unloaded (no R_3) voltage divider?

2. How does the output voltage (V_{out}) vary as you change the load (R_3) on the divider? Be as specific as possible.

3. How does the current required of the power supply (I) vary as you change the load (R_3) on the divider? Be as specific as possible.


4. How does the current *through* R_2 vary as you change the load? (Note $I_2 = V_{out} / R_2$)

5. Reflect on Sal Greco's saying, "You need enough I to keep the V across the R " in the context of this "loaded" voltage divider example.

Pre-Lab: Oscilloscope Orientation

Name: _____

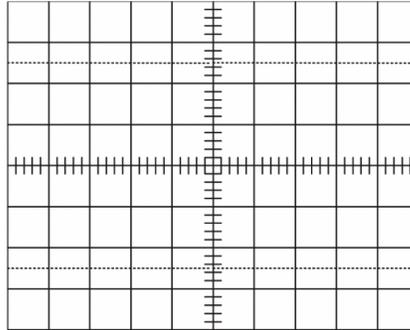1. Your 'scope is set to 0.2V/div and 5ms/div. Draw an example of the oscilloscope trace for a sine wave with amplitude 0.65V and period 30ms:




*Note that in this example, we have used the **maximum** Volts/div and Sec/div settings which still allow this (particular) complete waveform to be seen -- i.e. that make it "biggest" on the screen. Such settings allow us to make the **most accurate** readings of our signals, and should be used as a matter of **habit** when using the 'scope: **Always make the signal as "big" as possible, to get the most accurate readings.***

2. After hooking up your source to the scope on Channel 1, you see only a straight line rather than an AC signal. Which of the following could be the source of this problem?


- a) Selector switch set to "GND" instead of "AC"
- b) Channel selector set to "Ch2" instead of "Ch1"
- c) Time/Div switch set at too low (i.e. too fine) of a setting
- d) Bad scope lead
- e) Any of the above

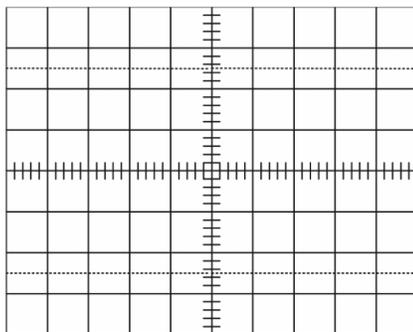3. Your input is a triangle wave of frequency 50Hz and amplitude 500mV. Decide on two different combinations of Volts/div and Time/div settings (which may or may not maximize the "size" of the image waveform), and draw the signal you'd see at each of these settings:



Volts/div: _____

Time/div: _____

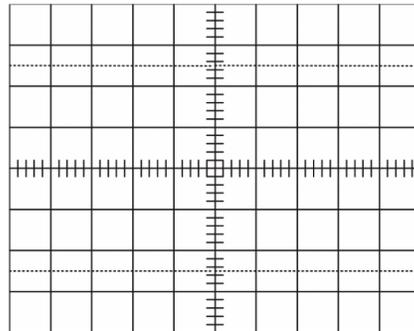

Volts/div: _____

Time/div: _____

4. Explain the effect on the oscilloscope trace of adjusting the **triggering level** and selecting the triggering slope. **Also**, describe the sort of picture are you likely to see if the trigger level is set at the maximum or minimum (i.e. amplitude) of a sinusoidal signal.

Lab: Oscilloscope Orientation

Name(s): _____


Purpose: To gain facility in the use of the oscilloscope for measuring properties of AC circuits

Equipment:

- Oscilloscope, e.g. BK Precision 2120
- Signal Generator
- Oscilloscope probe and/or something to go from BNC connector ('scope input) to banana plug (signal generator output)

Introduction/About the Scope:

The oscilloscope is essentially a voltmeter --- the voltage of a signal is directly linked to the voltage which causes electrons in the 'scopes cathode ray tube (CRT) to deviate in the vertical direction. The speed at which the electron beam sweeps across the screen is set by the "Time" (or "Sec/Div") knob. There are *lots* of knobs and switches on the scope. Their operation is described in our textbook and the 'scope manual. The *key* knobs and switches you'll be using are shown below:

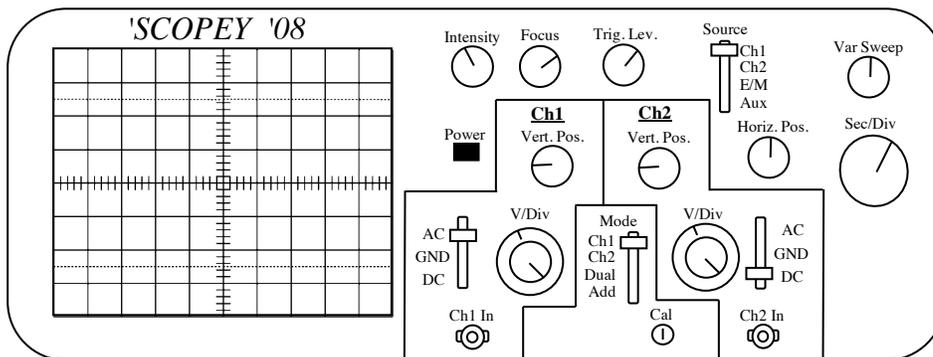

Our oscilloscopes are analog (as opposed to digital) scopes, and their operation is "manual"; that is to say, they do not automatically select the appropriate scale (so-called "auto scale") nor do they have an automated frequency analyzer to tell you what the frequency of your signal is. Rather, we will select our scales manually such that the **maximum** deviation of the scope trace is visible for a given voltage, and that no more than one (complete) period of oscillation is visible on the trace.

As a voltmeter, the oscilloscope has a very large **impedance**, (which is like resistance), meaning that it can be hooked up in parallel to a circuit element and very little current will flow. If, however, the circuit component you are measuring has itself a very large impedance (e.g. a 1M Ω resistor), **then hooking up the scope can distort the operation of the circuit you are trying to measure.** For *most* of the circuits we cover in this course, this will not be a problem, but you should keep this in mind whenever you are measuring a high-impedance source.

The two principal inputs on the scope are two BNC (bayonet Neil-Concelman) connectors. The BNC connector is a type of RF connector used for terminating coaxial cables. The cables we will use will terminate on the other end with either an **oscilloscope probe**, a pair of alligator clips, or a pair of banana plugs. For each of these "probe-like" ends, there will be a positive side and a "ground" side. Often you only need to use the positive side, because...

NOTE ABOUT OSCILLOSCOPE GROUND: The building's earth-ground is connected to the outside ring of each of the BNC probe connectors. This ground is also common to the ground wires of **both** input probes. So if you put the ground clips of the probe for Channel 1 and the probe for Channel 2 on two different parts of the circuit, the ground will **short** both of those points together.


Procedure:

1. Getting a Picture

Switch the oscilloscope on. Set triggering to channel 1 and make sure that the automatic triggering is on. Set the "Vert Mode" switch to Channel 1, "Source" to Channel 1. Set the "CH1" switch to "GND", and adjust the intensity and focus on the screen, and the "Vert Pos" knob for Channel 1, until you see a thin green line which runs along the exact center of the screen. Then change the "CH1" switch from "GND" to "AC".

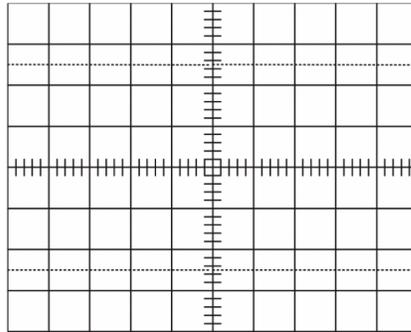2. Calibration

Connect the BNC connector of your probe to the Channel 1 input of your scope. Attach the + lead of the probe to the Calibration output of the scope. Set the Volts/div and Sec/div knobs to maximize the size of the signal trace ("picture") on the screen. Draw what you see (not what you think you "should" see!):



Volts/div: _____

Time/div: _____

What are the shape, amplitude and period of this signal?

Shape (sine, triangle, square?): _____

Amplitude: _____

Period: _____


Using the period, calculate the frequency. Frequency: _____

The signal should be a square wave of 1V amplitude ($= 2V_{pp}$), and frequency 1kHz, but perhaps your 'scope is not calibrated correctly. If your scope is not calibrated correctly, you **MUST** calibrate it before proceeding.

Calibrate it in the following way: Adjust the "little knob" inside the Volts/div knob until the amplitude of the wave appears as 1V. If the frequency is not 1kHz, adjust the "Var Sweep" knob, **and** please notify your instructor immediately.

3. Measuring General Signals

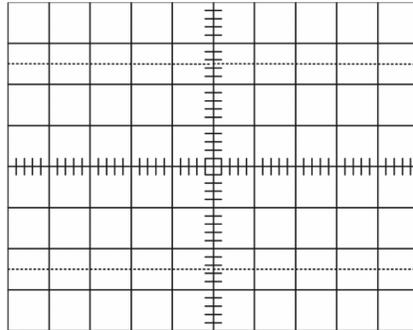3.1- With your signal generator turned off, hook up the input of the scope to the output of the signal generator. Turn the amplitude of the signal generator all the way the zero setting (which is all the way counterclockwise) and turn it on. Set the shape to sine wave, the frequency to 800Hz, and turn up the amplitude about a quarter turn (or less). Draw what you see:



Volts/div: _____

Time/div: _____

What are the amplitude and period of this wave?

Amplitude: _____ Period: _____

3.2 - The x5 switch - Now pull out the little knob in the middle of the Channel 1 Volts/Div knob. What happens to the picture? i.e., what changes and what does not change?

4. Additional Questions

4.1 - How would you measure a DC signal using an oscilloscope?

4.2 - We didn't talk about multi-channel input modes, e.g. X-Y mode, summing, and so forth. What would you like to learn about these, and in particular, what uses for multi-channel scope tracing might you find in audio engineering applications?

Lab: RC Circuits

Name(s): _____

Purpose: To observe the response of series RC circuits to both DC and AC sources.

Equipment:

- AC Signal Generator
- Oscilloscope and probe
- Resistor and a ceramic capacitors (e.g. 11nF)
- Computer with Excel
- Digital Multimeter

Part 1: DC Circuits

In this first part, we will investigate the charging and discharging of a capacitor in a DC circuit.

Procedure:


Select a capacitor and resistor, e.g. 11nF and 2200Ω, respectively. Measure the resistance and capacitance using a multimeter, and write them here:

R: _____ C: _____


Use these to compute the value of your *RC time constant* τ .

$\tau =$ _____.

Build the following circuit:

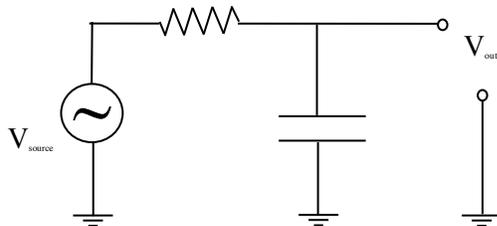

Use your signal generator as V_{source} and connect oscilloscope Channel 1 across it. Use Channel 2 as V_{out} , i.e. the voltage across the capacitor. Set the signal generator to square wave, with a period several times larger than your RC time constant, e.g. around 10 kHz. Set the scope to dual trace, triggering on channel 1. Set both Ch1 and Ch2 on the same number of volts/div, while maximizing the size of the waveform(s) --- you can set the "zero" to be a line near the bottom of the screen, rather than the center line. Draw a picture of what you see on Channel 2.

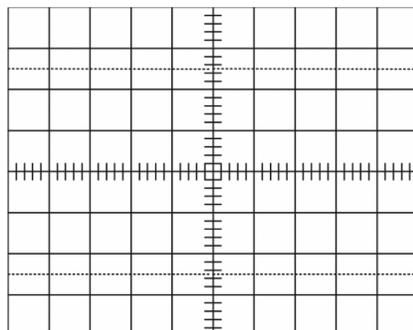

Settings:

V/div: _____

Sec/div: _____

Now, using the *discharging* phase of the oscillation, on Channel 2, take several values of the voltage at different times from at beginning of the discharge ($t=0$), and write them on the following table:

Time t	Voltage V
0	$= V_0$

We expect the discharge phase of the capacitor's cycle to go as $V = V_0 \exp(-t/\tau)$. Dividing by V_0 and taking the natural log of both sides, we find

$$\ln\left(\frac{V}{V_0}\right) = -\frac{1}{\tau} t.$$

Using Excel, make a graph of $\ln(V/V_0)$ vs. time. Fit a line to it and take its slope. The inverse of this slope will be a measure of your time constant τ .

τ (experimentally determined): _____.

Question:

How does this value of τ correspond to the value obtained at the beginning of the lab?

Part 2: AC Circuits - the Low Pass Filter

When the signal oscillates too rapidly, the capacitor does not have sufficient time to charge completely, resulting in a decreased output for the capacitor. The "turn-over" frequency at which this begins to occur is given by

$$f_0 = \frac{1}{2\pi\tau} = \frac{1}{2\pi RC}.$$

Calculate what you expect your turn-over frequency to be in Hz:

$f_0 =$ _____.

The general behavior or *amplitude response* from the filter is given by the *gain* G , which is the ratio of the output amplitude to the source amplitude:

$$G = \frac{A_{out}}{A_s} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_0}\right)^2}}$$

Procedure:

Now switch the signal generator to sine wave. Start the sine wave at a very low frequency $f \ll f_0$ and choose some input voltage, e.g. 1V (amplitude or peak-to-peak; just be consistent below...). For several *widely-spaced* values of the input frequency (**e.g. 20Hz to 90kHz**), record the output voltage. Record a few extra frequencies/voltage pairs around f_0 . Record them on the following table on the following page. (You may simply record the frequency reading from the signal generator.)

Frequency (Hz)	V_{out}
20	
90000	

Take your values and plot them on a *log-log plot* of V_{out} vs. frequency. If necessary, create extra columns in which to calculate $\log_{10}(f)$ and $\log_{10}(V_{out})$. Print out the graph and staple it to your report.

Questions:

Referring to your graph, what happens for $f < f_0$?

What happens for $f > f_0$?

And how would you describe the voltage output (or *gain*) near f_0 ?

Lab: Loudspeaker Impedance

Name(s): _____

Equipment:


- Two multimeters
- Loudspeaker
- Resistor, 5 – 30 Ohms, preferably 10 Ohms.
- Signal Generator

Recommendation: *Bring earplugs for this lab*


Background:

A loudspeaker presents a load which a combination of *inductive reactance* (due to the coil that makes up the electromagnet), *resistance* (due to the wire in the coil having a finite resistance), and *mechanical impedance* (due the mechanical process of pushing the cone in and out against air resistance). These three combine to form the overall speaker impedance Z_{Sp} .

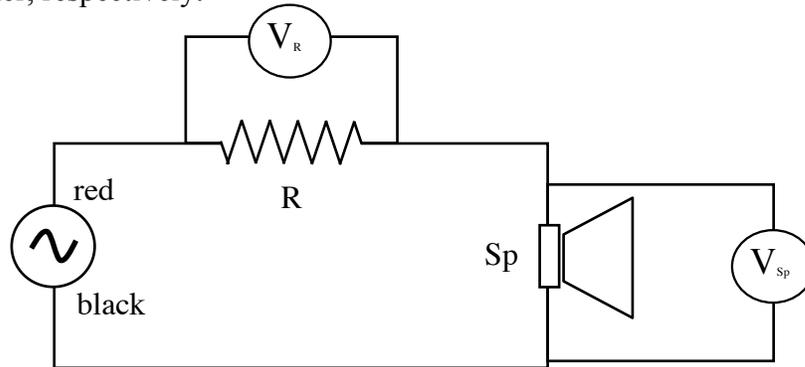In this lab, we will measure Z_{Sp} , the impedance of a loudspeaker, as a function of frequency. We will do this by placing it in series with a resistor R and measuring the voltages V_R and V_{Sp} across the resistor and speaker, respectively.



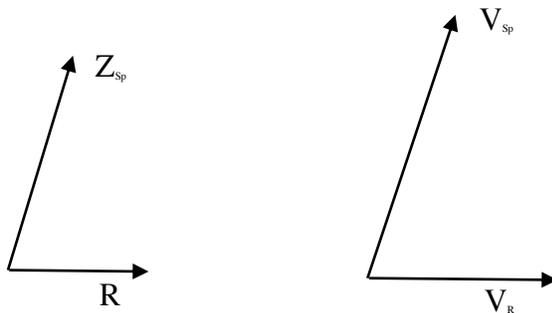With this information, we can compute Z_{Sp} by noting that the relative lengths of the voltage vectors are *similar* to the relative lengths of the impedances (think of the impedance diagram and voltage diagram), i.e. $R / V_R = Z_{Sp} / V_{Sp}$.



In other words,

$$Z_{Sp} = R \frac{V_{Sp}}{V_R}.$$

Procedure:

1. Before building the circuit, first use the ohmmeter setting on a multimeter to measure R , the resistance of your resistor, and (separately) R_{Sp} , the resistance of the loudspeaker:


$$R = \underline{\hspace{2cm}} \text{ Resistor,} \quad R_{Sp} = \underline{\hspace{2cm}} \text{ Speaker Resistance}$$

2. Now build the circuit: Place the resistor in series with the loudspeaker, and attach the signal generator across this combination, as shown in the schematic. Set both multimeters to AC volts. Place one meter across R to measure V_R , and the other meter across the speaker to measure V_{Sp} .
3. Turn the amplitude knob a quarter-way up on the signal generator.
4. By varying the frequency and reading voltages using the meters, record (simultaneous) values for V_R and V_{Sp} , for frequencies from 10 Hz to 10000 Hz, choosing frequency values that are farther spaced apart as you increase the frequency – you will ultimately be using a logarithmic scale for frequency. Note: Do not simply choose frequency values *a priori*, but rather choose your values as you follow the shape of the graph, getting multiple values below 100 Hz where it curves the most. Get 18 points in all.
Cautionary note: make sure to get at least 3 digits of precision for all measurements, especially for V_R .
5. Calculate Z_{Sp} , the impedance of the speaker for all frequencies, using the formula on the previous page.
6. Make a plot of Z_{Sp} vs. log frequency. (See sample data, below..)

Question(s):

1. How do the values of Z_{Sp} shown in your graph compare with the value of R_{Sp} ?
2. At what (“low”) frequency is the speaker impedance a *local* maximum?
3. Why do you think your speaker is “rated” at 8 Ohms by the manufacturer?

Sample Data:

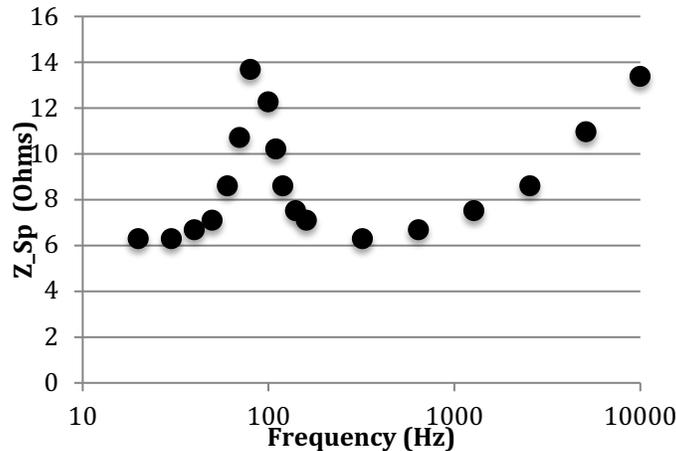

Quote: ‘A speaker is not linear 8 ohms at all frequencies. We did this [test] at Prince’s [studio]. The JBL 18” in the mains were rated at 600 watts 8 ohm, however the impedance dropped to 2 ohms at 60 Hz, flowing A LOT more power at 60 Hz. No wonder the JBLs were so punchy because they flowed over 2000 watts at 60 Hz. This is also why Prince could literally blow the cone out of the basket. I had 18 spares to keep 8 in service.’

*-- Sal Greco, Head Engineer, Belmont OceanWay Studios.
Formerly head engineer for Prince.*

Lab: Transformers

Purpose: To investigate the practical application of magnetic induction, become acquainted with the construction and operation of transformers.

Equipment:

- PASCO™ Basic Coil Set
- AC Power Supply / Signal Generator
- 2 Digital Multimeters
- Solderless Breadboard
- 8-Pin Iron Core Transformer
- Resistors of various values
- Wires w/ banana plugs
- Alligator clips

Part I: Transformer Construction


The ideal output of a transformer is given by the formula

$$V_2 = \frac{N_2}{N_1} V_1 \tag{1}$$


where V_2 is the secondary voltage, N_2/N_1 is the turns ratio of the transformer, and V_1 is the primary voltage. In real life, this ideal is rarely realized. In this section of the lab, we will see how close we can come to it, by varying the construction of the transformer.

Procedure:

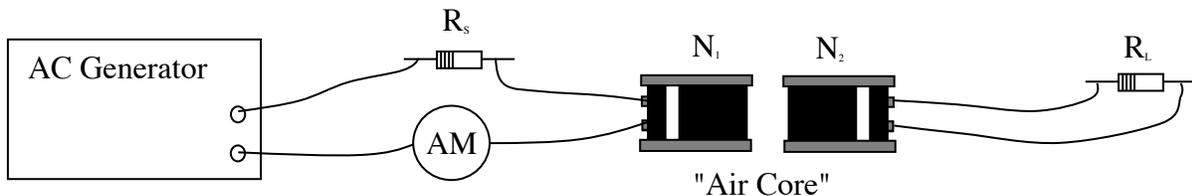
1. With the signal generator off, set the Digital Multimeter to AC Volts (20V range) and connect it to the signal generator. Turn the signal generator on, set it to sine wave and 1000 Hz. Adjust the amplitude of the AC source until it registers 6V on the multimeter. Turn off the signal generator and disconnect the multimeter.
2. Using wires & alligator clips, put a resistor of $R_s=100\Omega$ and an ammeter in series with the ($N_1=$)400-turn coil, and connect this combination across the signal generator.
3. Connect a resistance of approximately $R_L=100\Omega$ across another coil with turns N_2 . Using the other multimeter, measure the voltage V_1 across the primary coil (note that it won't be 6V due to the resistor), and then the voltage V_2 across the secondary. Record this on the data sheet provided.



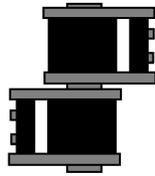
4. Make measurements for two different secondary coils, for the air core transformer shown above, as well as the following transformer configurations:



"Single Rod"

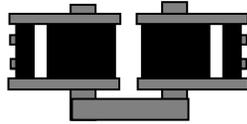

"U-Shaped"

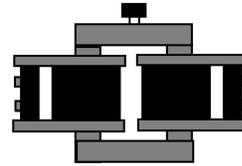


"Ring-Shaped"

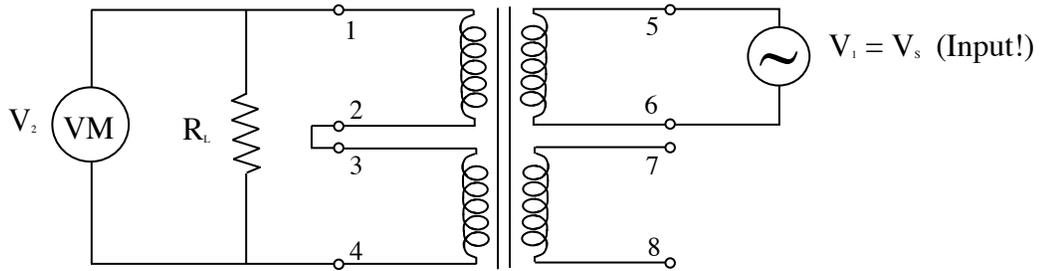5. Using your measurements of I_1 , your measurements of V_2 and your *measured* value of the resistor R_L (using the ohmmeter), calculate $I_2 (=V_2/R_L)$ and the ratio I_1/I_2 .

Part II: Frequency Response, using "Real" Transformers

We have a set of ring-shaped transformers which can be pressed into solderless breadboards. These transformers have eight leads, arranged and numbered from 1 to 8. We'll be using the transformer "backwards" and stepping *up* the voltage. Using jumper kits, connect leads 2 and 3 together. Hook the source voltage across leads 5 and 6, and the load resistance across leads 1 and 4. The following diagram shows the final configuration:



Fix the AC signal fixed at some voltage (or just leave it at 6V), press the "range" buttons on the signal generator to record the primary and secondary voltages for 10Hz, 100Hz, 1000Hz, and 10000Hz.

Part IV: Impedance Matching

$$\frac{N_2}{N_1} = \sqrt{\frac{Z_L}{Z_s}} \quad (2)$$

Depending on time, we may or may not be able to do this in lab. A separate handout will be distributed for this section if it is undertaken.

Transformer Lab Data Sheet Name(s): _____

Part I: Transformer Construction $R_s =$ _____ $R_L =$ _____

Core	N_1	N_2	V_1 (meas.) <i>Not 6V!</i>	V_2 calc'd, $=V_1 N_2 / N_1$	V_2 (meas.)	V_2 / V_1	I_1 (meas.)	I_2 $=V_2 / R_L$	I_1 / I_2
Air	400								
Air	400								
<i>Air, 90°</i>									
Rod	400								
Rod	400								
U	400								
U	400								
Ring	400								
Ring	400								

Questions:

1. How did varying the construction of the transformer affect its output?
2. How do your output voltage (V_2) values compare with the ideal expectation (Eq. (1))?
3. How did the ratios V_2/V_1 and I_1/I_2 compare?
4. Why do you think V_1 changed even though you weren't changing the amplitude of the source?

Part II: Frequency Response, using "Real" Transformers

$N_2 / N_1 =$ _____

Frequency (Hz)	V_1 (meas.)	V_2 (meas.)	V_2 / V_1
10			
100			
1000			
10000			

Question: How would you describe the frequency response of the transformer?

Lab : Diodes & DC Power Supplies

Name(s): _____

Purpose: To gain hands-on experience in constructing AC-to-DC power conversion circuitry using semiconductor components.


Overview: In this lab, we will start with a simple half-wave rectifier and build up to a DC power supply using a bridge rectifier and capacitive filter. We will also do some thinking about the use of voltage regulators!

Equipment:


- AC signal generator
- Oscilloscope and probe(s)
- Solderless breadboard
- 4 Diodes
- 1 Resistor, $\sim 100\Omega$ (doesn't really matter)
- 2 Capacitors: one "small" ($\sim 10\ \mu\text{F}$) and one "large" ($\sim 1\text{mF}$)

Part I: Half-Wave Rectifier

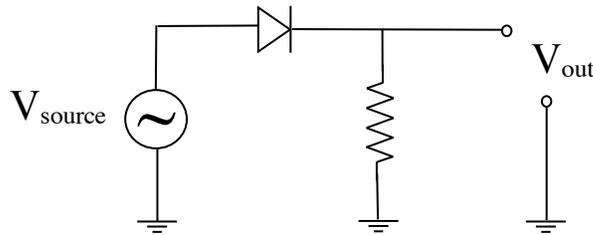Build the circuit below, and draw the source and output voltages on the grids provided. For the source voltage, use a sine wave with amplitude 10V at a frequency of 1kHz. Set the AC/GND/DC switch to "DC" on both scope channels.




V_{source} / Ch1

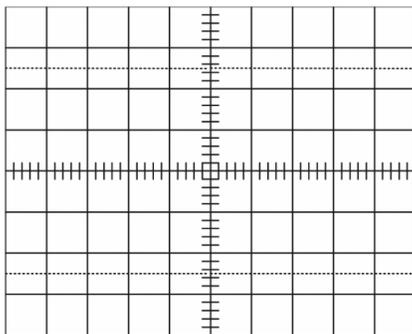

Volts/div: _____

Time/div: _____

V_{out} / Ch 2

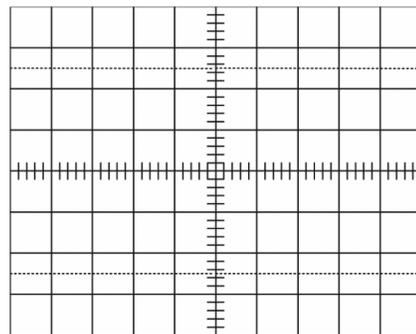

Volts/div: _____


Time/div: _____

Question:

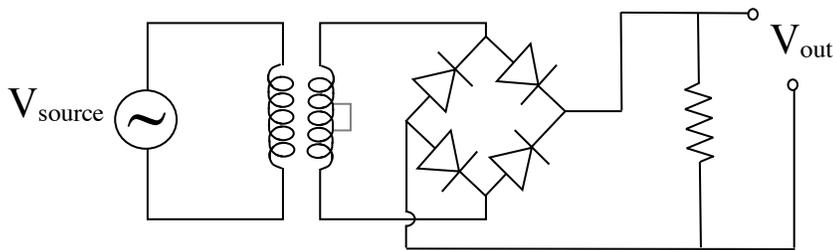
1. What do you measure the voltage drop across your diode to be?

Part II: Full-Wave Rectifier

Now construct the bridge rectifier shown below and, using the same source settings, graph the output voltage. Note: It's best to use a "step up" transformer to make sure there is plenty of voltage to drive the secondary circuit.



V_{out}

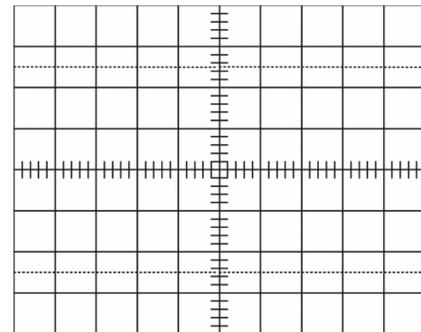


Volts/div: _____


Time/div: _____

Part III: Filtered Power Supply

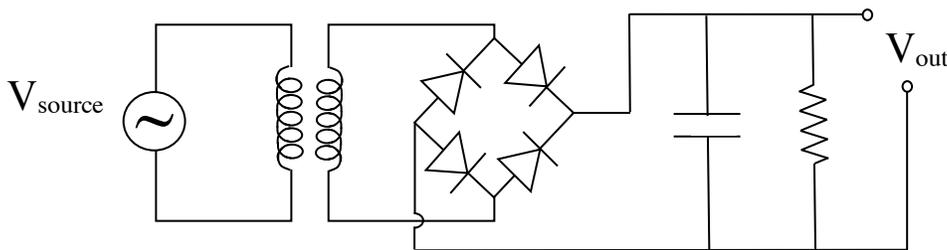Now insert a small capacitor to function as a "filter" in the circuit you just built, as shown below. Graph the output voltage. Then do the same for a larger capacitor.




V_{out} - Small C

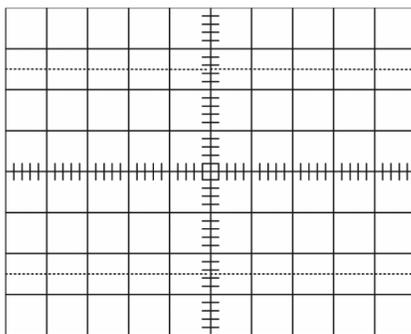

Volts/div: _____

Time/div: _____

V_{out} - Large C

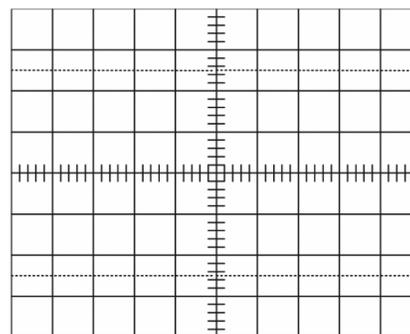

Volts/div: _____

Time/div: _____

Questions:


1. For the small capacitor, what is the maximum voltage obtained by the filtered full-wave signal? What is the minimum voltage?
2. What are the effects of increasing the capacitance in the filter?

Part IV: Thinking about Regulators

A voltage regulator can be a Zener diode or an integrated circuit (IC) regulator chip. It's designed to keep the voltage from *exceeding* a certain value, by allowing more current to flow through it at large voltage values and "shunting" it away from the load. If you don't put the minimum required voltage across the regulator, very little current will flow through it and, for the purposes of the power supply, it will function like an "open" circuit element. Put differently, *you need as much or more voltage across the regulator than it is rated, for it to do anything in your power supply.* So, for example, if you want a regulated 4.5V, you would need to supply 4.5V *or more* --- up to some limit; regulators are only rated to within a certain maximum voltage rating, beyond which they burn out

Question:

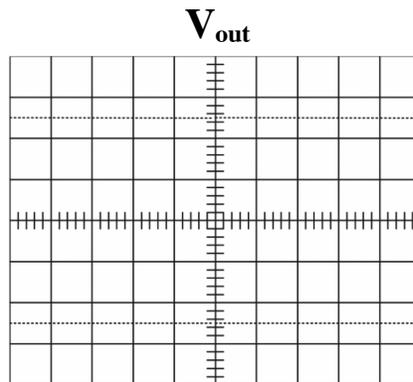1. Say you want to use a voltage regulator, but for some reason you don't include a capacitive filter before the regulator, and instead try to regulate the "bare" full-wave-rectified signal. Try to figure out what output you'd expect to see if the full-wave-rectified signal has a peak voltage of 5V and your regulator is rated at 3V, and graph this output below. (Assume a sine wave for the AC source voltage. *Hint: the regulator/Zener "cuts the top off."*)



Volts/div: _____

Lab: Transistors & Simple Amplifier

Name(s): _____


Purpose: To investigate the "variable resistor" properties of transistors, using them to construct a simple amplifier.

Equipment:

- Oscilloscope & two probes. (All voltage measurements will be made via the scope, e.g. in "DC" mode)
- Ohmmeter
- DC Power Supply
- AC Signal Generator
- Transistor
- Capacitor (any size)
- 4 resistors. (Suggested values: $R_1=560\Omega$, $R_2=100\Omega$, $R_c=560\Omega$, $R_e=100\Omega$)

Procedure:

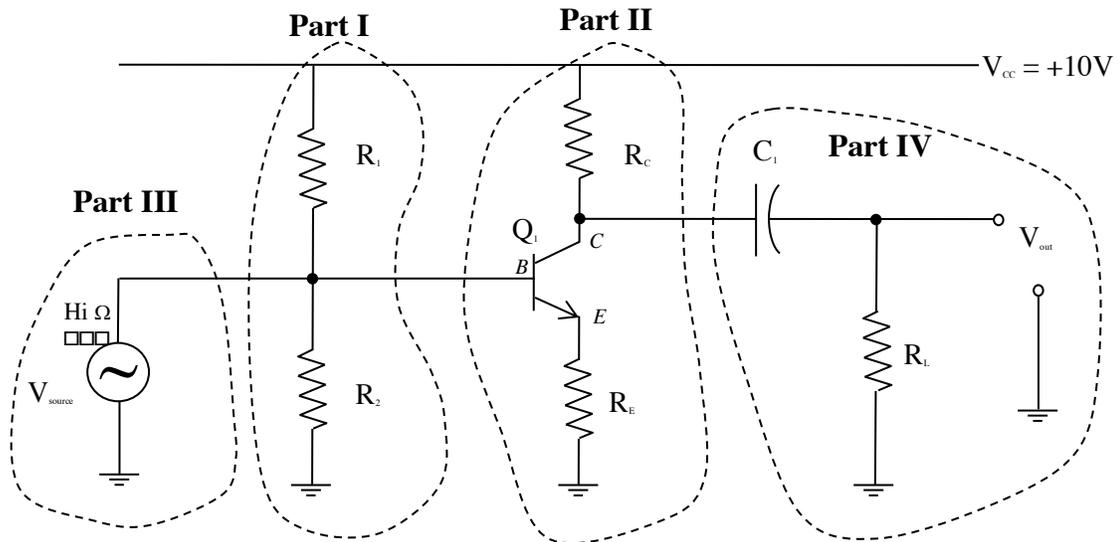We will build this amplifier, shown below, in a series of stages, labeled Parts I-IV.



I. Building the 1st Voltage Divider

We will operate the transistor within its "active region", i.e. with a base voltage somewhere in between 0V ("off") and V_{cc} ("saturation"). To do this, we will use a voltage divider (circled region in diagram) to bias the transistor's base ("B" in the diagram). To begin, we will **build only the voltage divider** part of the circuit. (Don't hook up anything else.) **Using your knowledge of voltage dividers** in DC circuits, and a supply voltage of 10V, select two resistors (R_1 and R_2) to produce a voltage across R_2 which is around $V_{cc}/4$. Write these *measured* resistor values below:

$R_1 =$ _____ $R_2 =$ _____

Build the voltage divider and *measure* the voltage across R_2 . This will be (roughly) the voltage at the transistor's base. Write that below:

$V_B =$ _____


II. Adding the "2nd Voltage Divider", i.e. the Transistor

We will now add a *second* voltage divider to the circuit, but this one will contain a transistor, which will function as a variable resistor, and will result in a *variable voltage divider*, where the output of this second divider is measured across Q_1 (the transistor) and R_E . To achieve this, you will need to select resistors R_C and R_E . The second "voltage divider" is *inverted*, so you want an R_C which is "large" (say 500Ω) and an R_E which is smaller (100Ω should suffice). Hook up the resistors and transistor to the power supply, taking care to match up the "E", "B" and "C" printed on the transistor with the appropriate parts of the circuit. Connect the base to the output of the first voltage divider. Your transistor should be on! Measure the voltage at the collector ("C" in the diagram), and write it below:

$$V_c = \underline{\hspace{2cm}}$$

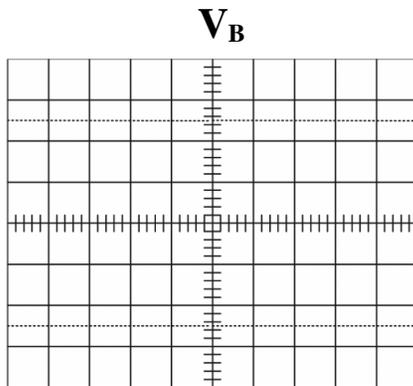
III. Supplying an AC Signal

Now connect the "high impedance" output AC signal generator to middle of the voltage divider. Thus we will add the AC sine wave to V_b , resulting in a varying voltage applied to the transistor. This will cause the transistor's resistance to vary, which will cause V_c to vary. Using the same DC settings for base and collector, draw the signal you see at these two terminals:



Volts/div: _____

Time/div: _____

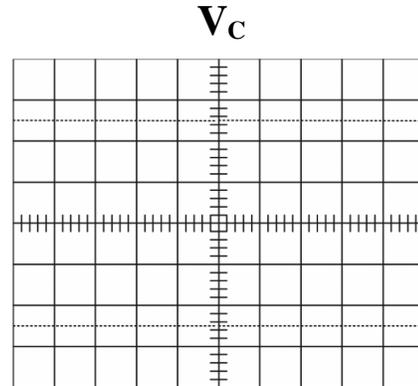

Volts/div: _____

Time/div: _____

IV. Stripping the DC Bias


Now we will add the capacitor and load resistor, as shown in the schematic. The load resistor should be large, 10K or more. The capacitor may be either an unpolarized or a polarized capacitor. If it is polarized, make sure you line up its polarity properly!

Question 1: We are looking at AC signals, and yet we may use a polarized capacitor, which requires current to always flow in the same direction. **Why** are we "okay" in using a polarized capacitor with our (amplified) AC signal?

Pre-Lab: Op-Amps

Name: _____

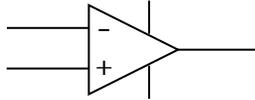5 groups. Answer 3 questions per group, and note where you found the information.



I. What is an Op-Amp?

1. Op-Amp is short for "operational amplifier". Why is this (latter) name used?
2. What does "IC" stand for, and what does it mean?
3. How does a differential amplifier work? What does a diff-amp consist of?
4. What are common mode input signals, and why might you want to reject them?
5. How many connections/terminals does an op-amp have, and what are they?
6. Explain the noise-rejecting feature of an op-amp and relate it to situations relevant to audio engineering technology.
7. What is a Darlington pair, and what is it used for?
8. Why do op-amps have so many transistors, i.e., are some of them used as "something else," and if so why?
9. Part of your IC op-amp is broken. What's your only troubleshooting option? Why?
10. What are offset nulls and what are they used for?

11. What is the common mode rejection ratio?

12. What does it mean for an op-amp to be a DC amplifier?

13. What are the three amplifier circuits ("sections") of an op-amp?

14. Explain the naming scheme (i.e. the model numbering/coding) for op-amps.

15. What are the three key characteristics of an op-amp? high ____, low ____, etc. Why are these qualities desirable?

Lab: Op Amp Circuits

Purpose: To gain hands-on experience with operational amplifiers and their applications.

Equipment:

- DC Power Supply
- AC Signal Generator
- 741 Op Amp
- Oscilloscope and probe
- Solderless breadboard and jumper wires
- Various resistors and a capacitor (e.g. 11nF)

Introduction:

We will build a closed-loop inverting amplifier, which has the following schematic:

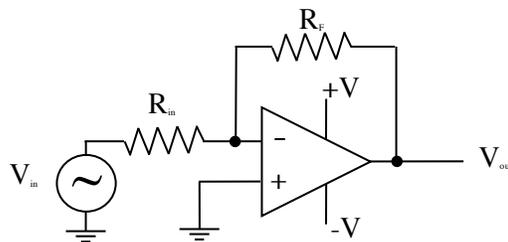


Figure 1: Closed-loop inverting amplifier diagram

The gain of the amplifier is **expected** to be $G = -R_f/R_{in}$, i.e. $V_{out} = -V_{in} R_f/R_{in}$.

"Offset Ground":

We'll "fool" the op amp into "thinking" we have DC power of $+V = 10V$ and $-V = -10V$ using a 20V power supply and a voltage divider, such that the middle of the voltage divider will serve as the "ground" (GND) for the op amp. Thus, the circuit we build is shown in Figure 2 -- but **don't build it yet!** Keep reading until the instructions tell you to build it.

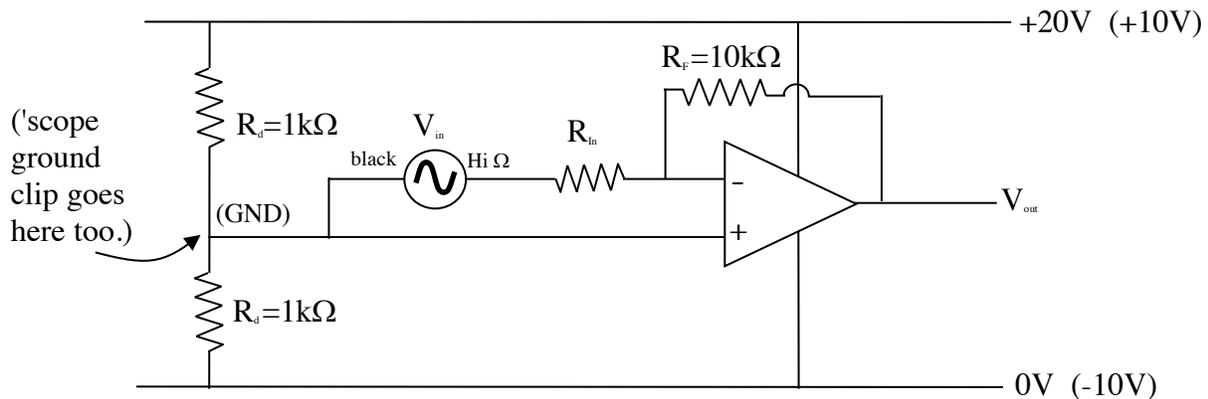


Figure 2: Using a positive DC power supply to "offset" a ground

In the figure above, quantities in parentheses show the voltage values relative to the op amp. All signals will be measured relative to "(GND)", i.e. relative to the ground *for the op amp*, not the ground of the DC power supply.

IC Wiring:

We'll be using a 741 IC op-amp, which is still one of the most common op amps in use today. The 741 has the following pin layout:

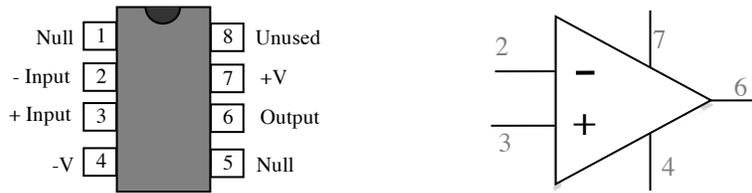


Figure 3: Pin layout for 741 IC op amp.


Note that the IC is just the right size to be turned sideways to "straddle" one of the wide spaces on our solderless breadboards, so that each pin on the IC gets its own 5-hole column of breadboard holes.

Closed-Loop Inverting Amp Procedure:

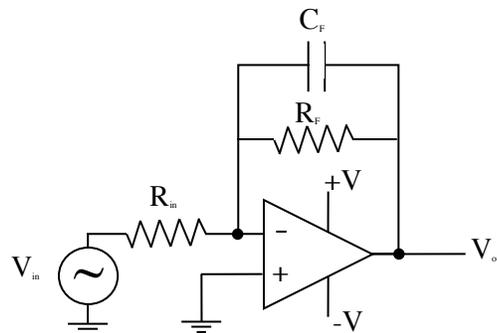1. Build the circuit shown in Figure 2, using $R_i=1k\Omega$, $R_f = 10k\Omega$. Use the nominal color-code values of R_{in} as shown in parenthesis on the data sheet (next page) to select your resistors, but use an ohmmeter and write in the *actual* values of the resistors.
2. Measure the input amplitude and output amplitude for various frequencies. From these compute the gain $G = V_{out} / V_{in}$; remember that an inverting amplifier has *negative gain*.

An Active Filter

Now we'll modify the circuit so that the feedback loop's impedance ($=R_f$ until now) will vary with frequency. That is, we will replace R_f with a reactive circuit element, namely a capacitor. The circuit will now look like



this:

Active Filter Procedure:

1. Add C_f (e.g., 11nF) in parallel with R_f , and use $R_{in} = 100\Omega$.
2. Answer the questions on the data sheet.
3. Measure the gain of the amplifier as a function of frequency, as indicated by the data sheet. Include a couple additional measurements near the turnover frequency.
4. Plot the gains vs. frequency using Excel.
5. Answer any additional questions on the data sheet.

Data Sheet: Op Amp Circuits

Name(s): _____

Closed-Loop Inverting Amplifier:

Frequency (Hz)	R_{in} (Ω)	Gain (Expected)	Input Amplitude (V)	Output Amplitude (V)	Gain (Measured)
1000	(1000)				
1000	(330)				
1000	(100)				
50	(330)				
50000	(330)				

Question 1: What do you notice about the behavior of the gain?

Question 2: What happens to the output when you remove the feedback resistor?

Active Filter:

Question 3: Do you expect this circuit to be a low-pass or a high-pass filter?

Question 4: If the turnover frequency were the same as that for a passive, series RC filter, what value would this frequency be?

Frequency (Hz)	Input Amplitude (V)	Output Amplitude (V)	Gain (Measured)
$E_s/10$			
100			
500			
1000			
1700			
4000			
10000			
50000			

Plot the Gain vs. Frequency for the measured gains of the active filter. Use a logarithmic scale for the both axes, i.e. plot $\log(|G|)$ vs. $\log(f)$. (Remember: "y vs. x".) Attach your graph to this sheet.

Question 5: How does gain of this filter differ from that of the passive ("regular") filter circuits we studied in the chapter on RC circuits?


Lab: Distortion!

The essence of distortion:

1. Clip the signal – “square-wave-ify”
2. Smooth for tone
3. Rock!

Part 1. Simplest Distortion

Two Diodes back to back, in parallel, will clip the signal on the top and bottom. Try that...

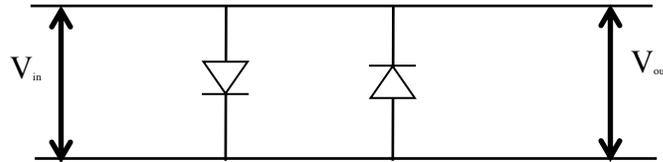


Part 2. Tone: Add a capacitor

In parallel. Try different values of capacitance!

Part 3. Add Amplification w/ Gain Control

URL: <http://www.circuitlab.com/circuit/4supth/distortion/>

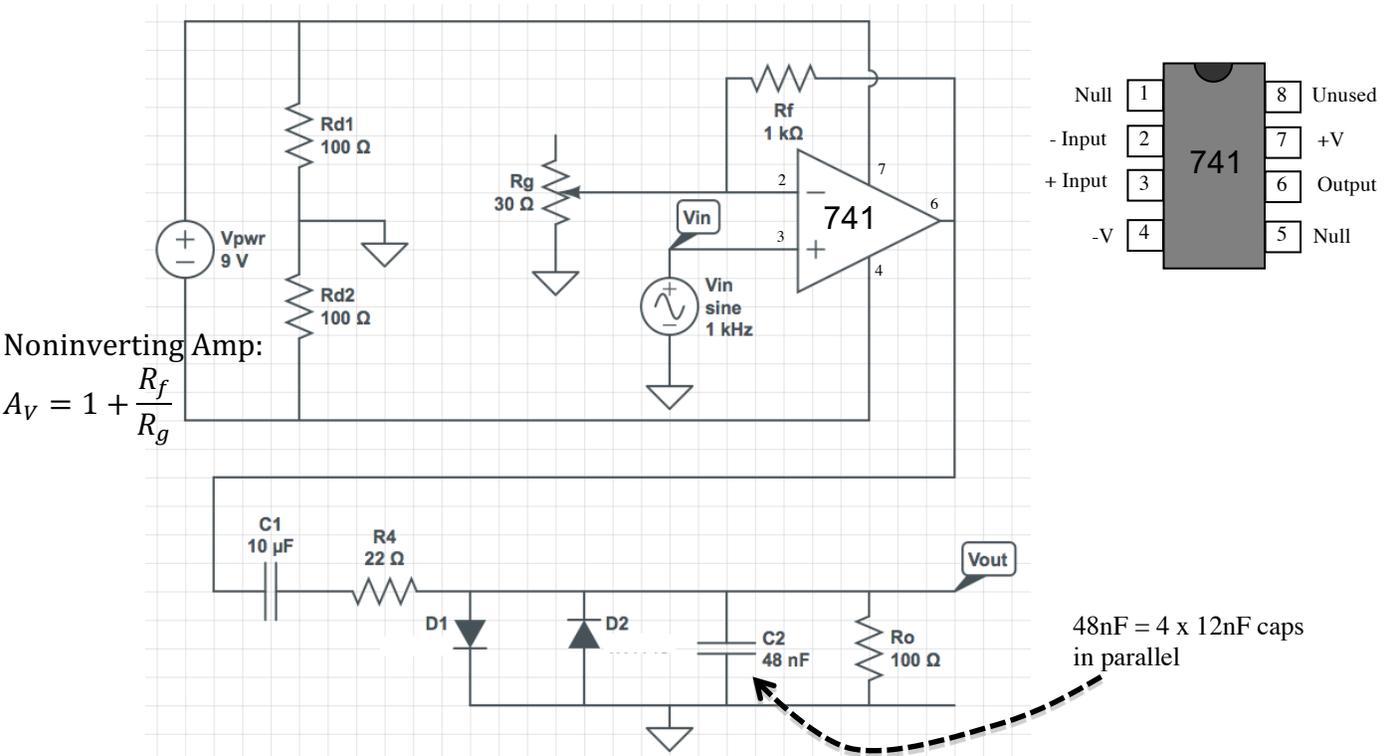

Part 4. Rock!

Replace V_{in} with guitar input, run V_{out} into an amp, and rock out!

Reference: Formulas & Prefixes

Current: $I = \frac{\Delta Q}{\Delta t}$ **Resistance:** $R = \rho \frac{\ell}{A}$ **Ohm's Law:** $V = IR$

Resistors: In series: $R_T = R_1 + R_2 + R_3 + \dots$ In parallel: $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

Power: $P = I^2 R = IV = \frac{V^2}{R}$

AC Signals: $f = \frac{1}{T}$ ω ("omega") = $2\pi f$ Amplitude $A = \frac{V_{p-p}}{2}$
 Sine waves: $V(t) = A \cos(\omega t + \phi)$ $V_{RMS} = \frac{V_{peak}}{\sqrt{2}}$ " V_{Avg} " = $V_{peak} \times 0.636$

Capacitors: $Q = CV$ Parallel plate: $C = \epsilon_0 \kappa \frac{A}{d}$ Reactance: $X_C = \frac{1}{\omega C}$ (-90 degrees)
 In series: $\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$ In parallel: $C_T = C_1 + C_2 + C_3 + \dots$

RC Circuits: Time constant: $\tau = RC$ Series Impedance: $Z = \sqrt{R^2 + X_C^2}$ Filters: $f_0 = \frac{1}{2\pi\tau}$
 Charging: $V(t) = V_{max}(1 - e^{-t/\tau})$ Discharging: $V(t) = V_{max}e^{-t/\tau}$

Faraday's Law: $V = -\frac{\Delta\Phi_B}{\Delta t}$, where $\Phi_B = BA$

Inductors: Reactance: $X_L = \omega L$ (+90 degrees)

Transformers: Turns ratio: $n = \frac{N_2}{N_1}$ Output: $V_2 = nV_1$ Impedance Match: $n = \sqrt{\frac{Z_L}{Z_S}}$

Op Amps: Closed-Loop Inverting Amp: $V_{out} = -\left(\frac{R_F}{R_{in}}\right)V_{in}$

Prefix	Abbreviation	Power of Ten	Example
Giga	G	10^9	1.21GW
Mega	M	10^6	10 MΩ
Kilo	K or k	10^3	20 kHz
Mili	m	10^3	4 mV
Micro	μ ("mu")	10^6	20 μA
Nano	n	10^9	100 nF

Student's Notes:

